



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S3 (S, FE) (FT/WP/S1 PT) Examinations May/June 2026 (2019 Scheme)

Course Code: EET201

Course Name: CIRCUITS AND NETWORKS

Max. Marks: 100


Duration: 3 Hours

PART A


Answer all questions. Each question carries 3 marks

Marks

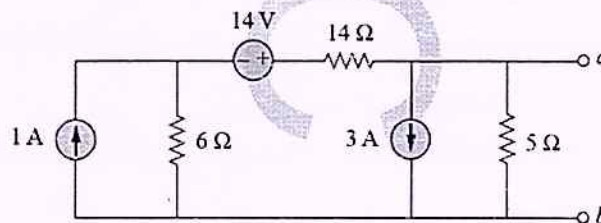- 1 Find the thevenin's equivalent circuit across the terminal a and b. (3)




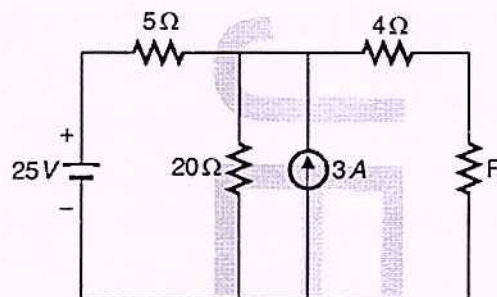- 2 Determine the value of R in the circuit shown for maximum power transfer. (3)




- 3 Determine the expression of current in an RL series circuit when a unit step input voltage is applied to it at time $t=0$ by means of a switch. (Inductor is initially relaxed). (3)

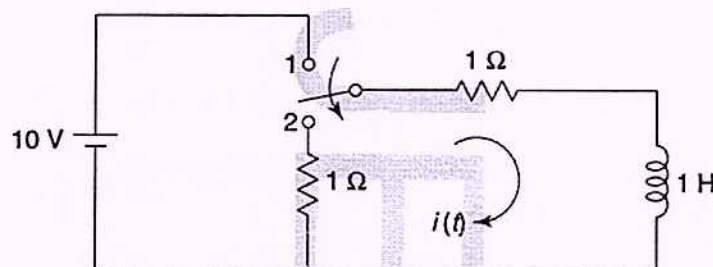- 4 In the network shown, the switch is moved from the position 1 to 2 at $t = 0$, steady-state condition having been established in the position 1. Determine $i(t)$ for $t > 0$. (3)



- 5 The combined inductance of two coils connected in series is 0.6 H or 0.1 H (3)
depending on relative directions of currents in the two coils. If one of the coils
has a self-inductance of 0.2 H, find (a) mutual inductance, and (b) coefficient of
coupling.

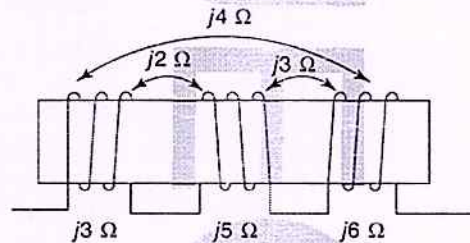- 6 Draw the dotted equivalent circuit and calculate the effective inductive (3)
reactance of the circuit shown.



- 7 Define resonance in RLC circuit. Plot the variation of current and impedance in (3)
parallel RLC circuit with frequency?

- 8 What is neutral shift. Explain with phasor diagram. What are its effects on the (3)
electrical system?

- 9 Prove that the overall transmission parameter matrix for cascaded 2 port (3)
network is simply the matrix product of transmission parameters for each
individual 2 port network in cascade.


- 10 Derive and represent h-parameters in terms of ABCD parameters. (3)

PART B


Answer any one full question from each module. Each question carries 14 marks

Module 1

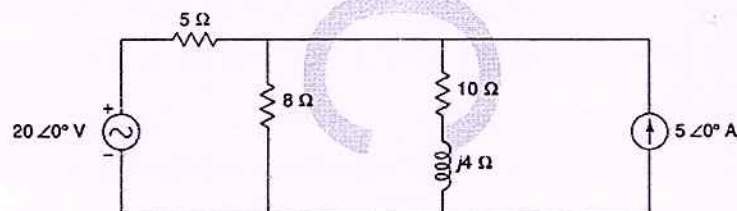
- 11 (a) Find the current through 8 ohm using Norton analysis. (8)



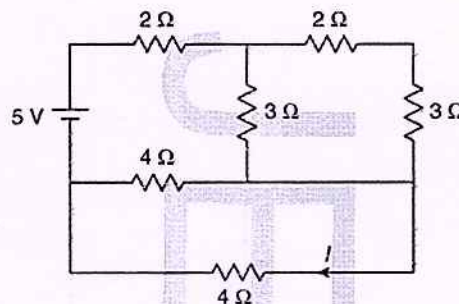
- (b) Verify the reciprocity theorem for the given circuit shown in Fig. (6)



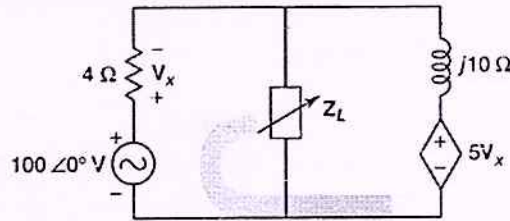- 12 (a) Determine the load Z_L required to be connected in the network for maximum power transfer and the value of maximum power. (8)




- (b) Determine the voltage across the $(2 + j5)$ ohm impedance for the network shown by using superposition theorem. (6)

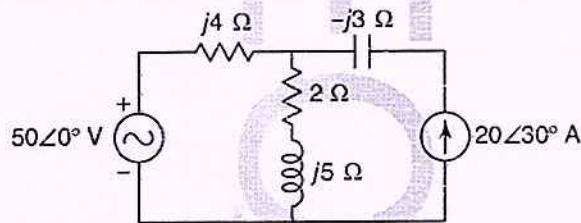


Module 2

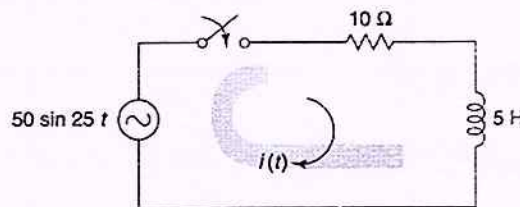- 13 (a) Obtain the current $i(t)$ shown in the network, when the switch is closed at $t=0$. (7)




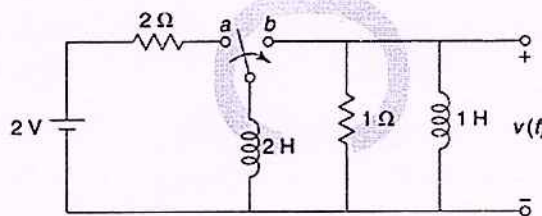- (b) The network of Fig. was initially in the steady state with the switch in the position a. At $t = 0$, the switch goes from a to b. Find an expression for voltage $v(t)$ for $t \geq 0$. (7)




- 14 (a) Derive the expression for current in an RC series circuit excited by an ac source. (7)

- (b) In the network of Fig., the switch is moved from a to b at $t=0$. Determine $i(t)$ and $v_c(t)$ (7)

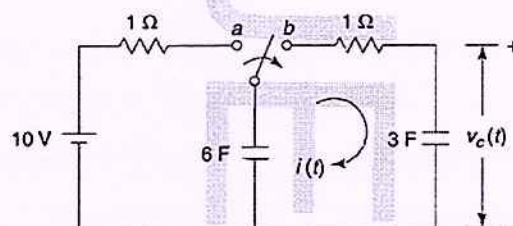


Module 3

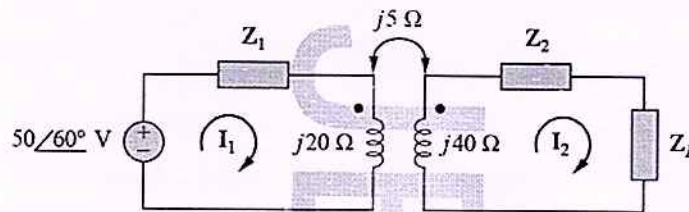
- 15 (a) Calculate the input impedance and current I_1 . Take $Z_1 = 60 - j100 \Omega$, $Z_2 = 30 + j40 \Omega$, and $Z_L = 80 + j60 \Omega$. (7)



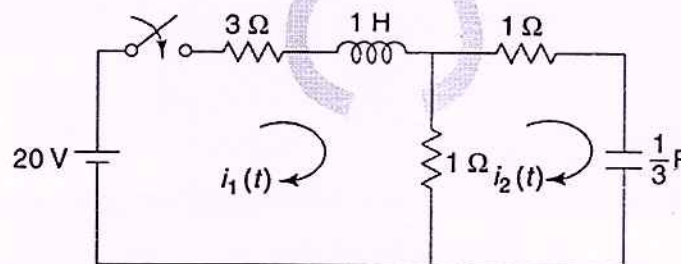
- (b) For the circuit shown, the switch is closed at $t=0$. Convert the circuit to its s transform and find the currents $i_1(t)$ and $i_2(t)$. (7)



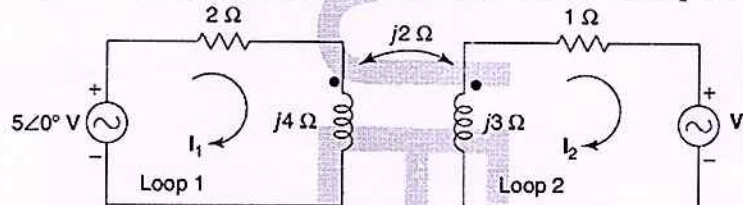- 16 (a) Find the voltage V_2 in the circuit shown such that current in loop 1 is zero. (8)




- (b) Draw the pole zero plot of the Impedance function $Z(s)$ shown in Fig. (6)

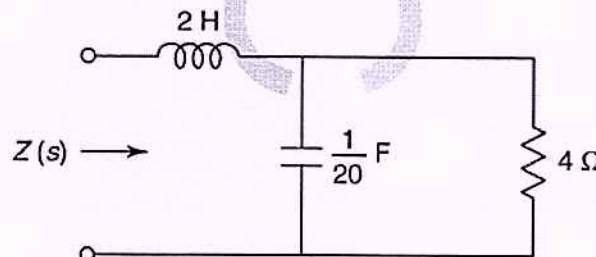

Module 4


- 17 (a) A Y connected alternator has 400V(line-line). It supplies a set of lighting loads (9)
at R, having phase impedance of $40 \angle 0 \Omega$, a capacitive load of $10 \angle -60 \Omega$ at
phase Y and an inductive load of $5 \angle 45 \Omega$ at phase B. The loads are connected
in delta. Obtain the phase current, line current and line voltages.

- (b) A series circuit comprising R, L and C is supplied at 220 V, 50 Hz. At resonance, the voltage across the capacitor is 550 V. The current at resonance is 1 A. Determine the circuit parameters R, L and C. (5)
- 18 (a) In a four-wire three-phase system, two phases have currents of 10 A and 6 A of lagging power factor of 0.8 and 0.6 respectively, while the third phase is open circuited. Calculate the current in neutral and sketch the phasor diagram. (7)
- (b) A $50\ \Omega$ resistor is connected in series with an inductor having internal resistance, a capacitor and 100 V variable frequency supply as shown in Fig. At a frequency of 200 Hz, a maximum current of 0.7 A flows through the circuit and voltage across the capacitor is 200 V. Determine the circuit constants. (7)

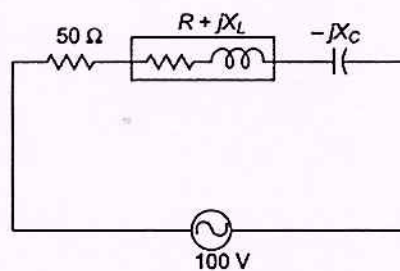


Module 5

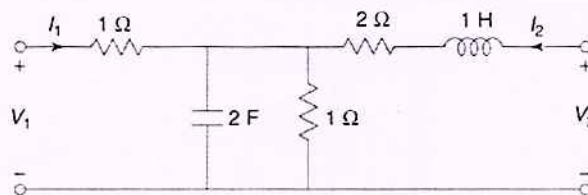- 19 (a) Find Z-parameter for the network shown in Fig. (7)



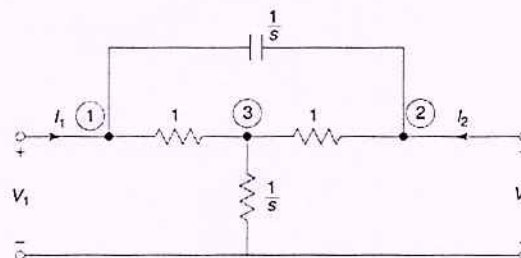- (b) Define ABCD parameters. Derive the condition for reciprocity and symmetry in terms of ABCD parameters (7)
- 20 (a) Obtain Y-parameters of the network shown in Fig. (7)



- (b) Find h-parameters for the network shown in Fig (7)

