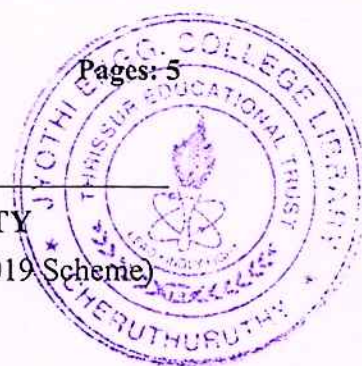


Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S3 (S,FE) (FT/WP/SIPT) Examinations May/June 2026 (2019 Scheme)



Course Code: ECT205

Course Name: NETWORK THEORY

Max. Marks: 100


Duration: 3 Hours

PART A

Answer all questions. Each question carries 3 marks

Marks

- 1 Explain super node analysis. (3)
- 2 Explain different types of dependent sources in electrical network. (3)
- 3 Explain the steps for finding Norton's equivalent circuit. (3)
- 4 State and explain reciprocity theorem. (3)
- 5 Find the initial and final values of the function whose Laplace transform is,
$$F(s) = \frac{(s+6)}{s(s+3)}.$$
 (3)
- 6 Mention the significance of poles and zeros of a network function. (3)
- 7 Obtain the expression for current when a unit step input is applied to a series RC circuit. (3)
- 8 Obtain voltage transfer function of the following network. (3)

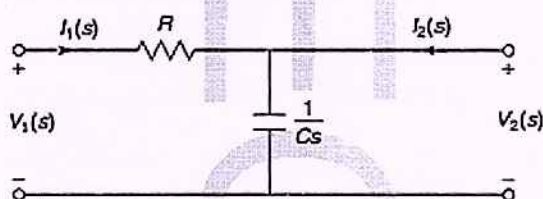


- 9 The impedance parameters of a two-port network are given as $\begin{bmatrix} 4 & 2 \\ 2 & 6 \end{bmatrix}$. Find the admittance parameters. (3)
- 10 Describe image parameters in connection with two port network. (3)

PART B


Answer any one full question from each module. Each question carries 14 marks

Module 1

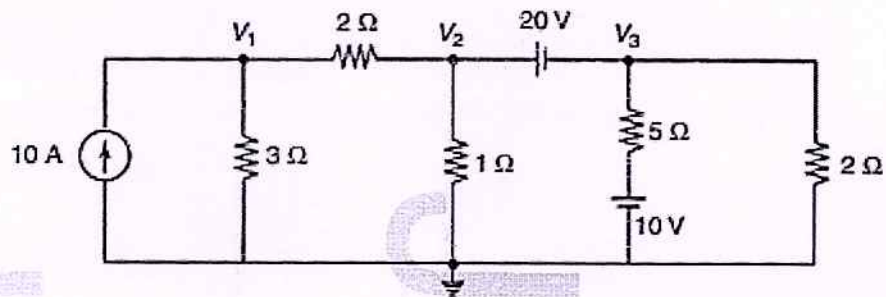
- 11 (a) Find the current through 5Ω using super node analysis. (7)



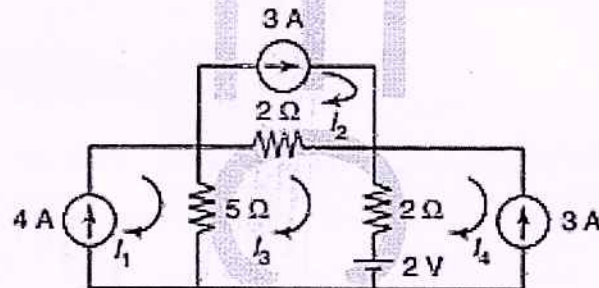
- (b) Determine the current through 5Ω in the given network using mesh analysis. (7)



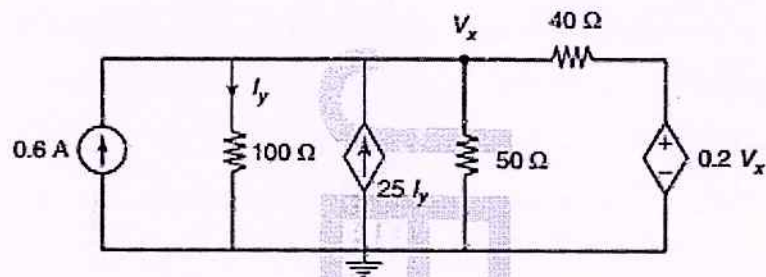- 12 (a) For the given network, find V_x using node analysis. (7)




- (b) Find the current through 10Ω using super mesh analysis. (7)

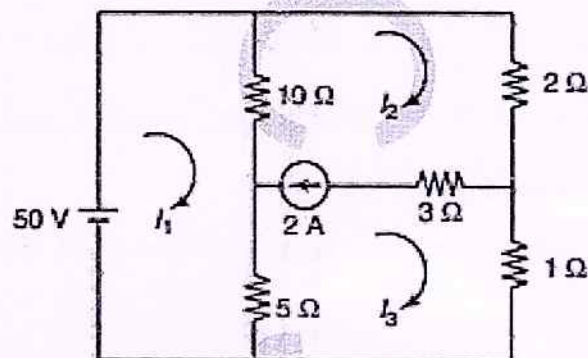


Module 2

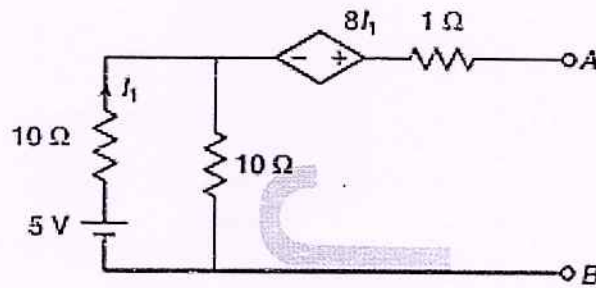
- 13 (a) Find the Thevenin equivalent of the given network. (7)



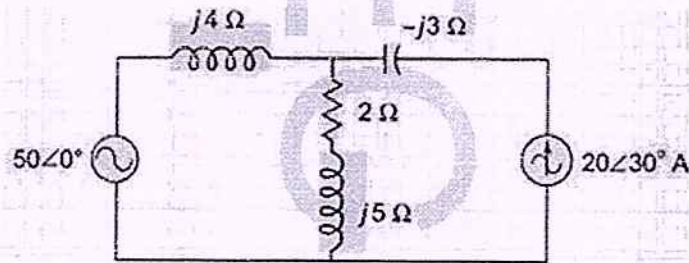
- (b) Determine the voltage across $(2+5j) \Omega$ for the network given below using superposition theorem. (7)



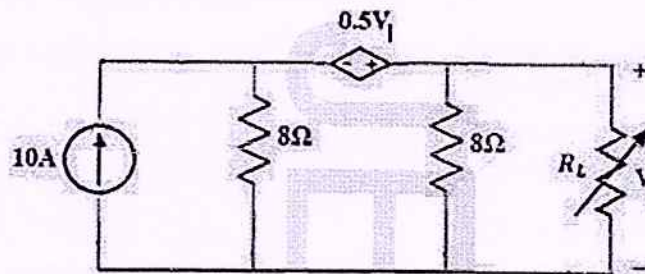- 14 (a) Determine the value of R_L for obtaining maximum power in the given network. (7)
Also evaluate the maximum power across the load.




- (b) Apply Norton's Theorem to find the current through 8Ω resistor in the given network. (7)

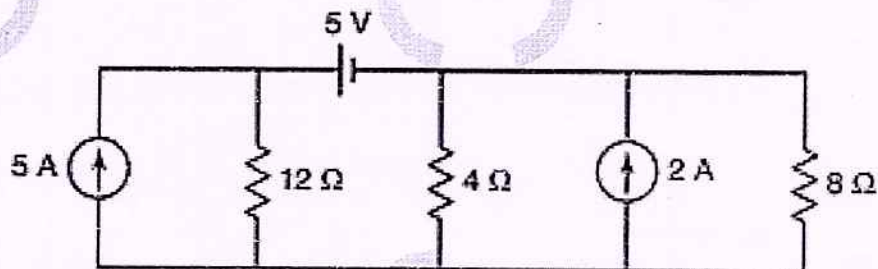


Module 3

- 15 (a) Verify initial and final value theorems for the following function, (7)
 $f(t) = e^{-t}(t+1)^2$.
- (b) In the given network, the switch is moved from position a to b, at $t = 0$. (7)

Find $v(t)$ for $t > 0$.

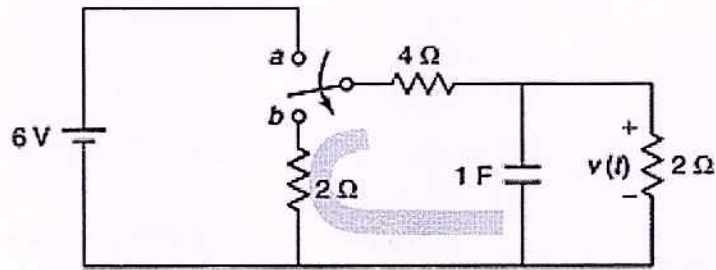

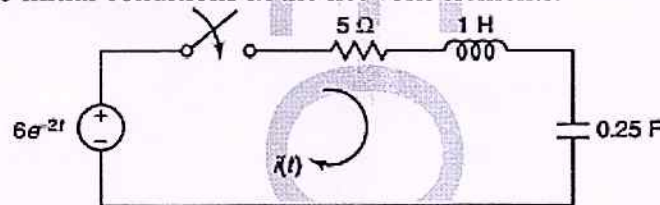- 16 (a) For the network shown, the switch is closed at $t = 0$. Determine the current $i(t)$ assuming zero initial conditions in the network elements. (7)



- (b) Find the expression for current through a series RL circuit when a pulse input of width 1s and amplitude 1V is applied across it. (7)

Module 4


- 17 (a) Draw the pole zero diagram of the following function and deduce the time domain response from it. (8)

$$V(s) = \frac{3s}{(s+2)(s^2+2s+2)}$$

- (b) What are the necessary conditions for transfer functions. (6)


- 18 (a) Sketch amplitude and phase response for $V(s) = \frac{s}{s+10}$. (8)

- (b) Find the network functions $\frac{V_1}{I_1}$, $\frac{V_2}{V_1}$ and $\frac{V_2}{I_1}$, for the network given below. (6)

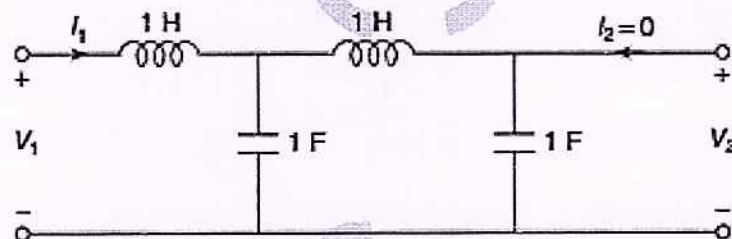


Module 5

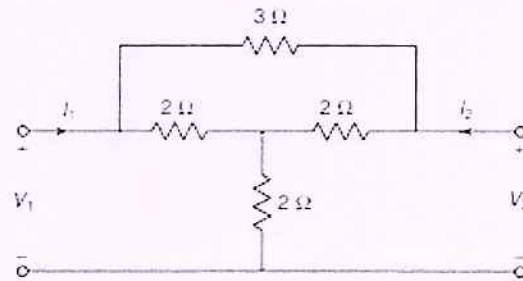- 19 (a) Find Y parameters for the given network. (8)



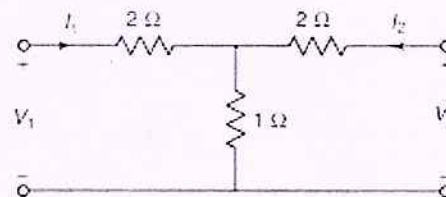(b) Obtain ABCD parameters in terms of Z parameters (6)

- 20 (a) Two identical sections of the given network are connected in series. Obtain the Z parameters of the overall connection. (6)



(b) Derive the conditions for reciprocity and symmetry for Z parameters and for ABCD parameters. (8)
