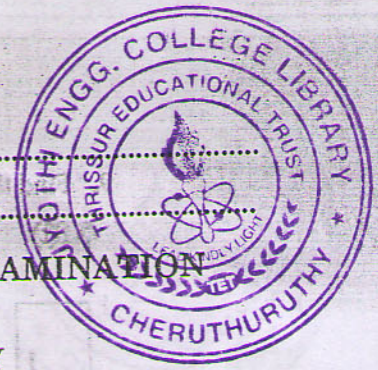


D 10039

(Pages : 4)

Name.....

Reg. No.....



THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION
DECEMBER 2010

EE09 303/PTEE 09 302—ELECTRIC CIRCUIT THEORY
(2009 admissions)

Time : Three Hours

Maximum : 70 Marks

Part A

(Answer all questions: 5 x 2 marks = 10 marks)

1. For the circuit shown in figure (1), find the power delivered by 1A source.

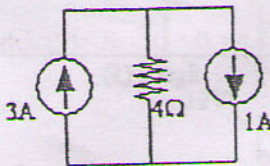


figure (1)

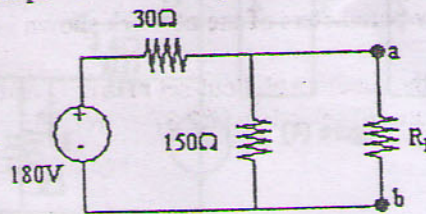


figure (2)

2. Find the load resistance R_L that will result in maximum power delivered to the load circuit shown in figure (2).
3. Use final-value theorem to find $f(\infty)$ if $F(s) = \frac{(s+2)}{s(s+3)(s+4)}$.
4. A resistive T network has 3Ω resistances in each series arm and 4Ω resistance in shunt arm. Find Z-parameters.
5. An admittance function is given by $Y(s) = \frac{s}{s+1}$. Realize the RC network.

PART B

(Answer any four questions: 4 x 5 marks = 20 marks)

6. Find I_b using mesh analysis for the circuit shown in figure (3).

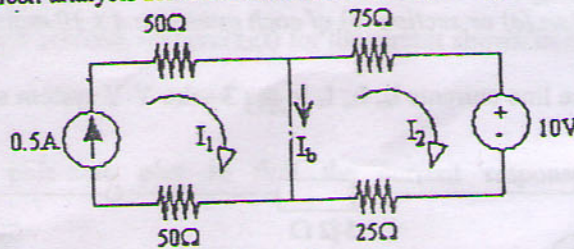




figure (3)

7. The three phase voltages of a 3-phase system are $V_a = 230\angle 0^\circ V$; $V_b = 210\angle -110^\circ V$ and $V_c = 190\angle 110^\circ V$. Determine the sequence components V_{a1} , V_{a2} and V_{a0} .

8. By using convolution theorem, determine the inverse Laplace transform of $F(s) = \frac{1}{s^2(s+1)}$.


Turn over

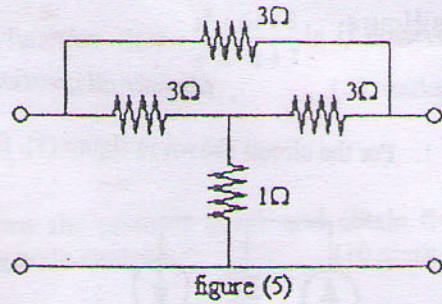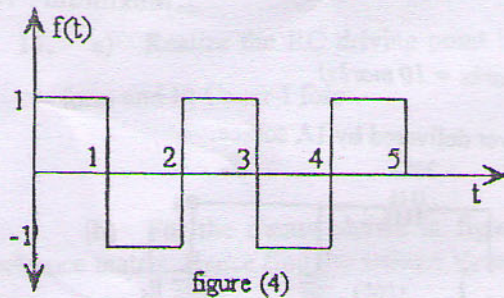9. Find the Laplace transform of square wave shown in figure (4).



10. Find y-parameters of the network shown in figure (5).

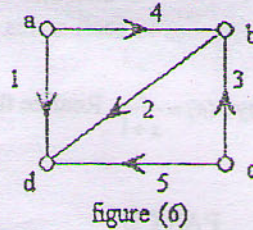
11. Find the fundamental cut-set matrix Q and tie-set matrix B for the oriented graph shown in figure (6) selecting {1,2,3} as tree. Hence, prove that $QB^T=0$.



PART C

(Answer section (a) or section (b) of each question: 4 x 10 marks = 40 marks)

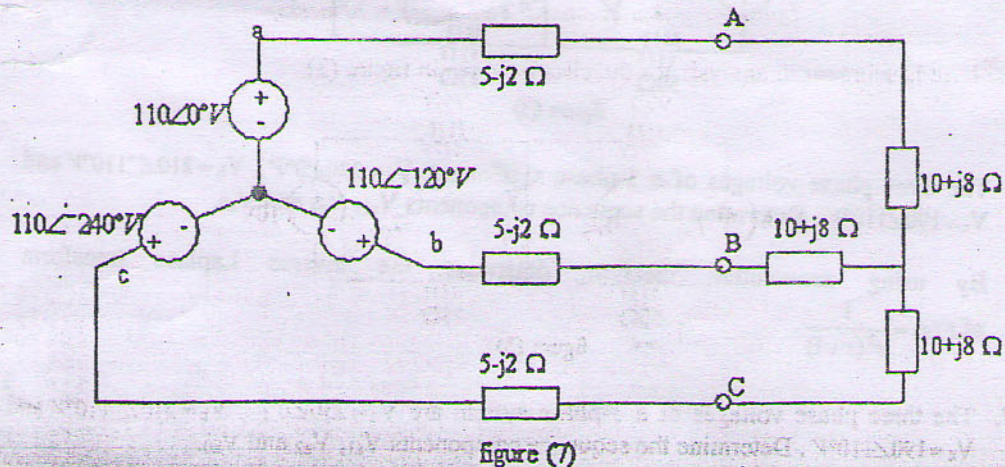12. (a) i) Calculate the line currents I_a , I_b , I_c in the 3-wire Y-Y system shown in figure (7). (5 marks)



- ii) A coil having a 2Ω resistance is connected in series with a $50\mu\text{F}$ capacitor. The circuit resonates at 100Hz . What is the inductance of the coil? If the circuit is connected across a 100V , 100Hz ac source, find the power dissipated in the coil. (5 marks)



- (b) Use Superposition theorem to find current I in the circuit shown in figure (8). (10 marks)

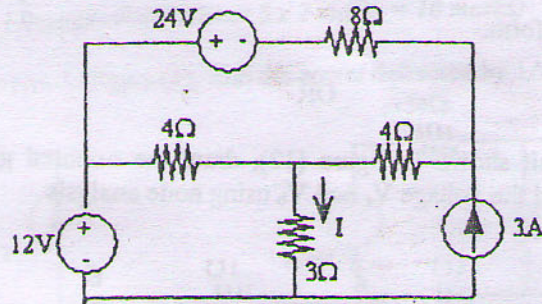


figure (8)

13. a) i) For the circuit shown in figure (9), determine the current through the 2Ω resistance when the switch is moved from position 1 to position 2 at $t=0$. The switch has been in position 1 for a long time to get steady state values. (5 marks)

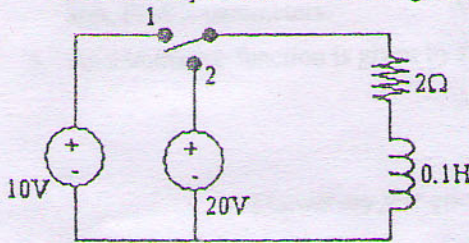


figure (9)

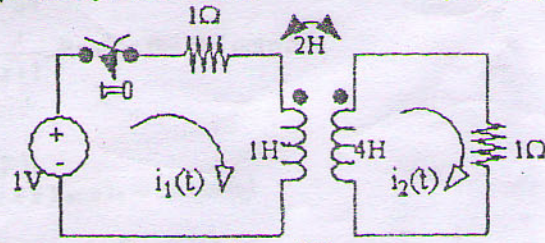


figure (10)

- ii) Find the currents $i_1(t)$ and $i_2(t)$ for the circuit shown in figure (10). (5 marks)

OR

- b) i) Use pole-zero plot to find the current response in time-domain if $I(s) = \frac{4s}{(s+2)(s+5)}$. (5 marks)

- ii) Find the driving point impedance of the network shown in figure (11). (5 marks)

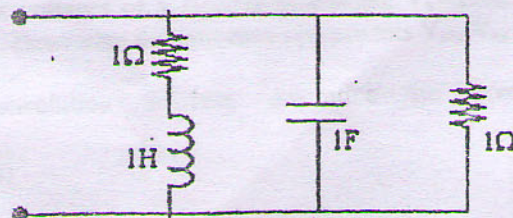


figure (11)

14. a) i) Find the open circuit and short circuit parameters of a T-network with resistance in each arm equal to 3Ω and hence find the image impedances. (5 marks)
ii) Derive the condition for reciprocity of a two-port network in terms of Z-parameters. (5 marks)

Turn over

OR

b) Design T and π networks of m-derived high pass filter having nominal characteristic impedance $R_0 = 900\Omega$, cut-off frequency $f_c = 2\text{kHz}$ and infinite attenuation frequency $f_a = 1.8\text{kHz}$. (10 marks)

15. a) Realize the RC driving point impedance function $Z(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$ in i) Foster-I form and ii) Cauer-I form. (10 marks)

OR

(b) For the circuit shown in figure (12), draw the oriented graph and obtain the incidence matrix. Hence find the voltage V_a and V_b using node analysis. (10 marks)

