

14990

Name:

Reg.No.



COMBINED I & II SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2010

EC 04108 - BASIC ELECTRONICS
(Common for EC, BM, BT, AI and IC)

Time : Three Hours

Maximum: 100 Marks

- I
- (a) Write a note on Electrostatic and Magnetic deflection sensitivities.
 - (b) Briefly explain the principle of operation of a triode.
 - (c) Explain the colour coding of resistors.
 - (d) Draw the DC equivalent model of a transistor and give its analysis.
 - (e) What is a Q point? Explain.
 - (f) Calculate the stability factor for a potential divider biasing circuit.
 - (g) Draw the circuit of a Half Wave rectifier and its waveforms. Also explain its principle of operation.
 - (h) Explain the operation of a series voltage regulator.

(8×5 = 40)

- II. (a) Derive an expression for the motion of an electron in
- (i) Uniform electric field
 - (ii) Transverse magnetic field.
- (OR)
- (b) (i) With block diagram explain the operation of a CRO. Derive an expression for its deflection sensitivity.
- (ii) With block diagram, explain the operation of a multimeter.

- III. (a) (i) Compare the characteristics of various types of capacitors.
- (ii) Draw the circuit of a clipper and clamper and explain its operation.

(OR)

- (b) Explain the operation and applications of
- (i) Common Emitter
 - (ii) Common Collector
 - (iii) Common Base
- Configurations.

- IV. (a) Discuss in detail about the various resistor biasing circuits.

(OR)

- (b) Discuss in detail about the operation of a Bipolar function transistor with its characteristics.

- V. (a) Derive the expressions for PIV, DC O/P voltage, ripple factor, efficiency and rectification factor of a full wave rectifier.

OR

- (b) (i) What is the need for filters in rectifiers? Explain.
- (ii) Explain the analysis of capacitor filters for rectifiers.

(15×4 = 60)
