

D 20921

(Pages : 2)

Name.....

Reg. No.....

**FIFTH SEMESTER B.TECH. (ENGINEERING) DEGREE  
EXAMINATION, OCTOBER 2011**

AI 09 505—POWER ELECTRONICS

(2009 Admissions)

Time : Three Hours

Maximum : 70 Marks

**Part A**

*All questions compulsory.  
Each question carries 2 marks.*

1. What is a Triac ?
2. Define Power Factor. What is the desirable value for it ?
3. What is an IGBT ?
4. What is a DC chopper ?
5. Draw the block diagram of the UPS.

(5 × 2 = 10 marks)

**Part B**

*Answer any four questions.  
Each question carries 5 marks.*

6. Briefly describe the structure of a thyristor.
7. Explain the operation of a Silicon Controlled Rectifier.
8. How to improve the power factor of a single phase and three phase converters ?
9. Explain the vector control of induction motor.
10. Explain the principle of operation of a Step Down chopper.
11. Design a simple drive circuit for a Power BJT.

(4 × 5 = 20 marks)

**Part C**

*Answer any four questions.  
Each question carries 10 marks.*

12. (a) Explain the structure and operation of a MOS Controlled thyristor (MCT) ?

(Or)

- (b) Discuss the static and dynamic characteristics of a GTO.

Turn over

13. (a) Explain the design of a Single phase and three phase converter circuit.

(Or)

(b) Discuss the design of a AC voltage controller circuit.

14. (a) Explain the principle of operation of a MOSFET/IIGBT chopper.

(Or)

(b) Explain in detail about the Mc-Murray Bedford inverter.

15. (a) With neat sketch, explain the operation of a :

(i) Switched Mode Power Supply.

(ii) Buck Boost Regulator.

(Or)

(b) Explain the applications of Microprocessors and Micro controllers in the control of Power Electronic circuits.

(4 × 10 = 40 marks)