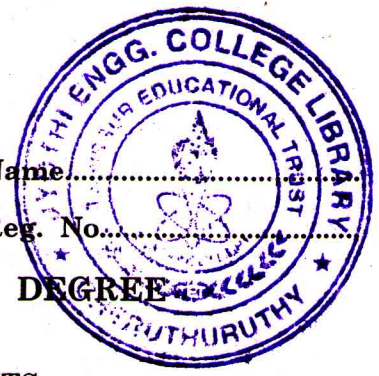


D 23427-A

(Pages : 2)

Name .....

Reg. No. ....



**FIFTH SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION, DECEMBER 2011**

**EC 04 503—LINEAR INTEGRATED CIRCUITS**

(2004 admissions)

Time : Three Hours

Maximum : 100 Marks

*Answer all questions.*

1. (a) Derive the gain due to an inverting and a non-inverting operational amplifiers.
- (b) Give one practical application of the following circuits :—
  - (i) Instrumentation amplifier.
  - (ii) Schmitt trigger.
  - (iii) Voltage comparator.Also define the parameter slew rate.
- (c) Write notes on switched capacitor filters.
- (d) What are active filters ? Write the salient features of Butterworth and Chebyshev filters.
- (e) What are three terminal voltage regulators ? Define the terms line regulation and load regulation.
- (f) Explain the principle of operation of a weighted resistor DAC.
- (g) Explain the working of a basic PLL using a block diagram.
- (h) Define the following terms :—
  - (i) Lock range.
  - (ii) Capture range.
  - (iii) Monostable multivibrator.

(8 × 5 = 40 marks)

2. (a) (i) Explain the various frequency compensation techniques adopted in an operational amplifier. (11 marks)
- (ii) Explain the working of a summing amplifier. (4 marks)

*Or*

- (b) Explain the working of :
  - (i) Wein bridge oscillator. (9 marks)
  - (ii) Antilog amplifier. (6 marks)

**Turn over**