

D 23522

(Pages : 3)

Name.....

Reg. No.....

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION
DECEMBER 2011**

EE 04 306—ELECTRIC CIRCUIT THEORY

(2004 Admissions)

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

Part A

1. (a) Explain the unbalanced delta connected load of 3 ϕ system.
- (b) A 400V, 3 ϕ supply feeds an unbalanced three wire star connected load. The branch impedances of the load are $Z_R = (4 + j8) \Omega$, $Z_Y = (3 + j4) \Omega$ and $Z_B = (15 + j20) \Omega$. Find the line currents (RYB).
- (c) Write a note on delayed standard time function.
- (d) The transform of current is $I(s) = \frac{2s}{(s+1)(s+2)}$. Sketch its pole-zero plot and obtain time domain response $i(t)$.
- (e) Design a low pass filter (both π and T section) having a cut-off frequency of 2 kHz to operate with a terminated load resistance of 500 Ω .
- (f) Derive the expression of ABCD parameters in terms of z parameters.
- (g) Find the network for the function $Z(s) = \frac{(s+1)(s+3)}{(s+2)(s+6)}$ using Cauer I form.
- (h) Short note on 'fundamental circuit'

(8 \times 5= 40 marks)

2. (a) Explain 3 wire and 4 wire systems in detail with diagrams. (15 marks)

Or

- (b) A delta-connected three-phase load has 10 Ω between R and Y, 6.36 mH between Y and B, and 636 μ F between B and R. The supply voltage is 400V, 50 Hz. Calculate the line currents of RBY phase sequence.

(10 marks)

- (c) Short note on 'sequence coupling'. (5 marks)

Turn over

3. (a) State and prove (i) Initial value theorem ; (ii) Final value theorem ; (iii) Convolution theorem of Laplace transform.

(7 marks)

- (b) For the following network in Fig. 1,

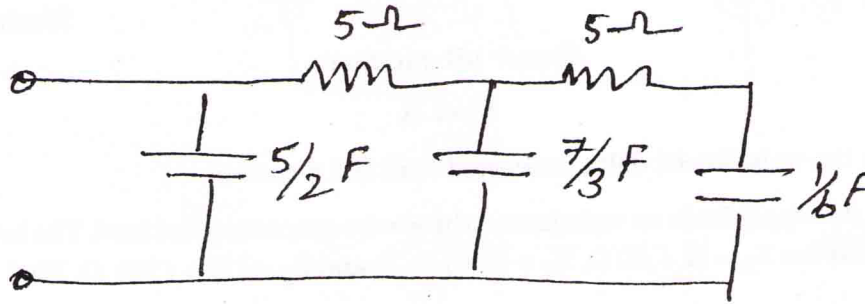


Fig. 1

Find $Z(s)$ and plot pole-zero diagram.

(8 marks)

Or

- (c) Using convolutional integral, find the Laplace inverse of, $F(s) = \frac{2(s+2)}{(s^2+4)^2}$.

(7 marks)

- (d) Find the driving point admittance function $Y(s)$ and sketch pole zero plot Fig. 2

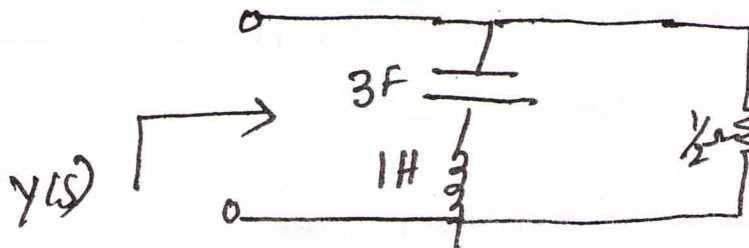


Fig. 2

(8 marks)

4. (a) Explain the interconnection of two port networks in detail.

(15 marks)

Or

- (b) Derive the equation of filter networks.

(15 marks)

- 5 (a) Obtain the state equation of the network shown in Fig 3.

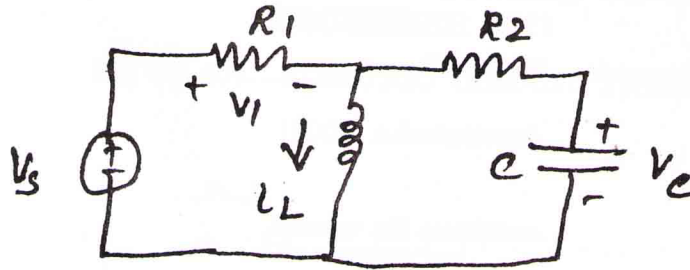


Fig. 3

- (b) Short note on 'properties of RL network function'.

(10 marks)

(5 marks)

Or

- (c) The driving impedance of a one port LC network is given by $Z(s) = \frac{3(s^2 + 1)(s^2 + 16)}{5(s^2 + 9)}$.

Obtain the second Foster form of an equivalent network.

(8 marks)

- (d) Select a tree and write the Fig 4 :

(i) Tie-set matrix

(ii) Cut-set matrix

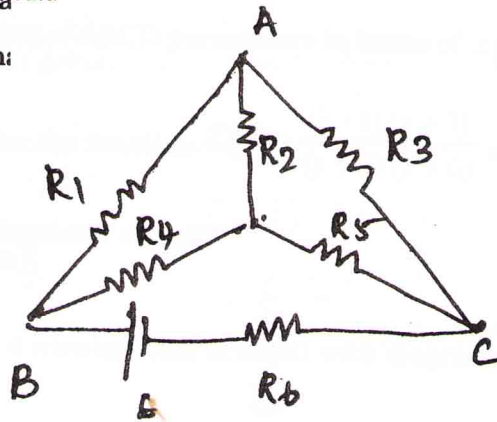


Fig. 4

(7 marks)

[4 × 15 = 60 marks]