

D 30904

(Pages : 3)



**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION  
OCTOBER 2012**

Electronics and Communication Engineering

EC 09 303/PTEC 09 302—NETWORK ANALYSIS AND SYNTHESIS

(2009 Admissions)

Time : Three Hours

Maximum : 70 Marks

**Part A**

Answer all questions.

1. State superposition theorem.
2. Draw the circuit diagram of a passive integrator.
3. State necessary conditions for a driving point function.
4. What is a constant K-filter ?
5. Test whether the polynomial  $P(s) = s^4 + s^3 + 4s^2 + 2s + 3$  is Hurwitz.

(5 × 2 = 10 marks)

**Part B**

Answer any four questions.

1. Find current through each resistor in the circuit using Nodal analysis for Figure (1).

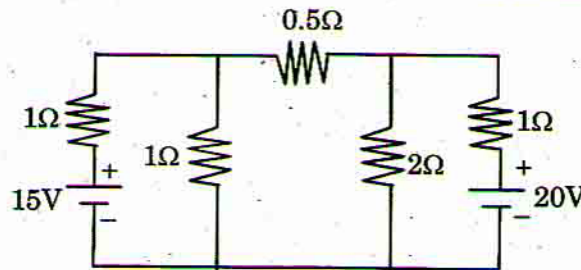


Fig. 1.

2. Find driving point admittance  $Y(s)$  for network shown in Figure (2).

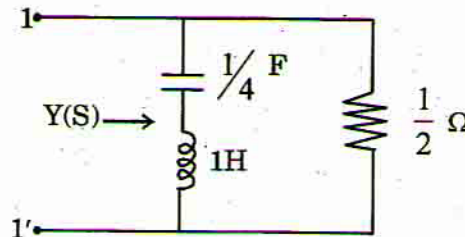


Fig. 2.

Turn over

- List out the properties of positive real functions.
- Find Z parameters for the network shown in Figure (3).

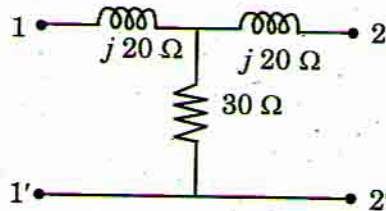


Fig. 3.

- Explain various types of filters.
- Obtain the pulse response of a series RC circuit.

(4 × 5 = 20 marks)

**Part C***Answer one question from each module.***MODULE I**

- A ramp voltage  $V = 5r(t - 2)$  is applied in a series RC circuit. Find the response if  $R = 1 \Omega$  and  $C = 0.25$  Farad.

(10 marks)

*Or*

- Find the power loss in the  $10 \Omega$  resistor using Mesh analysis in Figure (4).

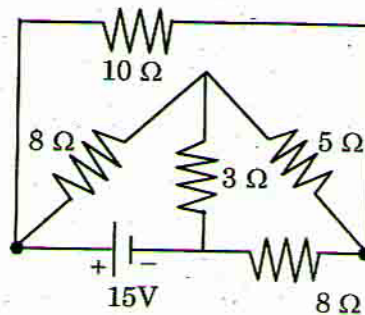


Fig. 4.

(10 marks)

## MODULE II

3. Given transform current in a network as  $I(s) = \frac{s}{(s+2)(s^2+2s+2)}$ . Draw the pole-zero plot and obtain time domain response.

(10 marks)

Or

4. Obtain Y-parameters of network shown in Figure (5).

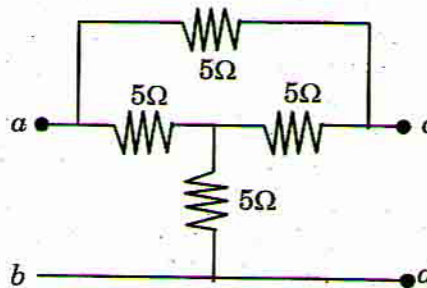


Fig. 5.

(10 marks)

## MODULE III

5. Synthesize a Chebyshev low pass filter to meet the specifications : Load resistor  $R_L = 600 \Omega$ ,  $\frac{1}{2}$  dB Ripple within pass band, cut off frequency  $5 \times 10^5$  rad/sec. and at  $1.5 \times 10^6$  rad/sec. Magnitude must be down to 30 dB.

Or

6. Transform a low pass filter into high pass filter.

## MODULE IV

7. Given  $Z(s) = \frac{s^4 + 7s^2 + 9}{s(s^2 + 4)}$ . Realize LC network using Cauer forms I and II.

(10 marks)

Or

8. Synthesize the given impedance function  $Z(s) = \frac{(s+2)(s+4)}{(s+1)(s+5)}$  using Foster Forms I and II.

(10 marks)

[4 × 10 = 40 marks]