 


**D 30906**

(Pages : 2)

Name: \_\_\_\_\_

Reg. No: \_\_\_\_\_



**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION  
OCTOBER 2012**

Electronics and Communication Engineering  
EC 09 305/PTEC 09 304—DIGITAL ELECTRONICS  
(2009 Admissions)

Time : Three Hours

Maximum : 70 Marks

**Part A**

*Answer all questions.*

1. Simplify the Boolean function  $F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ .
2. What are universal gates ?
3. Perform  $1010100 - 1000011$  using 1's and 2's complements.
4. Draw the JK flip-flop with truth table.
5. Write the difference between sequential circuits and combinational circuits.

(5 × 2 = 10 marks)

**Part B**

*Answer any four questions.*

6. Simplify in sum of products and product of sums

$$\overline{A}\overline{C} + \overline{B}D + \overline{A}CD + ABCD.$$

7. Draw a NAND logic diagram that implements  $F(A, B, C, D) = \sum(0, 4, 12)$ .
8. Implement  $F(A, B, C) = \sum(1, 2, 4, 5)$  with a multiplexer.
9. Give the excitation tables of JK, SR and T flipflops.
10. What is ring counter ?
11. Write the importance of ASM chart with example.

(4 × 5 = 20 marks)

Turn over

## Part C

Answer section (a) or section (b) of each question.

12. (a) Simplify the Boolean function  $F(A, B, C, D, E) = \sum(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$  and implement using minimum number of NOR gates.

Or


- (b) Explain Quine Mc Cluskey method with an example.
13. (a) Draw the logic diagrams of a look ahead carry generator and 4-bit full adder with look ahead carry and explain the operations.

Or

- (b) Explain the working of (i) TTL NAND gate and (ii) ECL gate with neat diagrams.
14. (a) (i) Construct a Mod-10 counter. (5 marks)
- (ii) Construct a 4-bit up-down counter. (5 marks)

Or

 - (b) Explain the working principle of universal shift register with neat diagrams. (10 marks)
15. (a) A sequential circuit has three flip-flops A, B, C ; one input  $x$  and one output  $y$ . The state diagram is given in Fig (1). The circuit is to be designed by treating the unused states as don't care conditions.
- (i) Use D flip-flops in the design.
- (ii) Use JK flip-flops in the design.



Or

- (b) Design a counter with the following repeated binary sequence using T flip-flops.

- (i) 0, 1, 2, 3, 5, 6.
- (ii) 0, 1, 3, 7, 6, 4.

(4 × 10 = 40 marks)