

D 32969

(Pages : 2)

Name.....

Reg. No.....

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE
EXAMINATION, DECEMBER 2012**

Electrical and Electronics Engineering

EE 04 305 – ELECTRONICS – I

(2004 Admissions)



Time : Three Hours

Maximum : 100 Marks

Answer all questions.

Part A

- I. (a) Write short note on diffusion capacitance of a diode.
(b) Compare E-MOSFET and D-MOSFET.
(c) Explain with relevant diagrams, the working of a bridge rectifier.
(d) Explain the working of a double limiter circuit.
(e) Explain thermal runaway.
(f) Compare small signal and large signal operation of amplifiers.
(g) Explain the importance of by-pass capacitor in amplifier.
(h) Write a short note on typical frequency response of an amplifier.

(8 × 5 = 40 marks)

Part B

- II. (a) In an open-circuited step-graded $p-n$ junction, derive expression for the contact difference potential.
(b) Explain the V-I characteristics of a $p-n$ junction diode.

(8 + 7 = 15 marks)

Or

- (c) Explain the construction and characteristics of CB-BJT.
(d) Explain the features of Schottky barrier junction.

(10 + 5 = 15 marks)

Turn over

- III. (a) Explain with relevant diagrams, the circuit of a full-wave rectifier. Derive the expressions for ripple factor, efficiency and TUF.

(15 marks)

Or

- (b) Compare LC and RC filters.
(c) Explain with necessary diagrams, the working of positive and negative damper.

(7 + 8 = 15 marks)

- IV. (a) Draw the h -parameter equivalent circuit of CE-BJT and derive the expression for current gain, input resistance, voltage gain and output admittance.

(15 marks)

Or

- (b) Explain with necessary diagrams, the working of a class-B push-pull amplifier. Also obtain value of maximum conversion efficiency.

(15 marks)

- V. (a) Draw the hybrid-Pi model for transistor in CE configuration and explain the meaning of each component.

(15 marks)

Or

- (b) Explain the operation of a differential amplifier and define the terms :

- (i) Common mode gain.
(ii) Differential mode gain.

- (c) What is a current mirror?

(10 + 5 = 15 marks)

[4 × 15 = 60 marks]