

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION  
DECEMBER 2012**

Electrical and Electronics Engineering

EE 04 306—ELECTRIC CIRCUIT THEORY

(2004 Scheme)

Time : Three Hours

Maximum : 100 Marks

**Part A**

- I. 1 A three-phase delta connected load has  $Z_{ab} = (100 + j0) \Omega$ ,  $Z_{bc} = (-j100) \Omega$  and  $Z_{ca} = (70.7 - j70.7) \Omega$  are connected to a balanced 3-phase 400 V supply. Determine the line currents  $I_a$ ,  $I_b$  and  $I_c$ . Assume the phase sequence  $abc$ .
- 2 A three-phase three-wire 300 V ACB system feeds the unbalanced Y-connected load shown in Fig. 1 Find the line currents and the phase voltages of the load. Also determine the displacement neutral voltage  $V_{ON}$ .

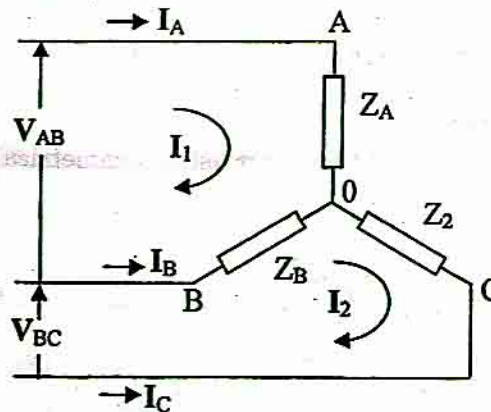


Fig. 1

- 3 Find the Laplace inverse of  $\frac{1}{s(s+4)}$  using convolution integral.

- 4 Realize the following reactance function in four canonic forms

$$\frac{(s^2 + 1)(s^2 + 6.25)(s^2 + 25)}{s(s^2 + 4.5)(s^2 + 9)}$$

- 5 Determine the transmission parameter A of the network in Fig. 2.

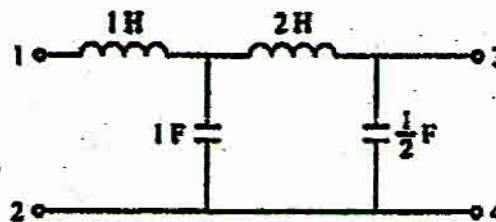


Fig. 2

Turn over

- 6 If a T section of a constant  $k$  low pass filter has series inductance 85 mH and shunt capacitance  $0.025 \mu\text{F}$ , calculate its cut-off frequency and the nominal design impedance  $R_0$ .
- 7 Check whether the polynomial  $s^4 + s^3 + 7s^2 + 4s + 6$  is Hurwitz or not.
- 8 Draw the oriented graph of the network in Fig. 3 and write the incidence matrix.

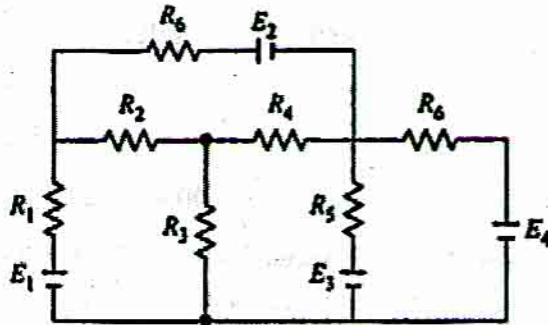


Fig. 3

(8 × 5 = 40 marks)

**Part B**

- II. (a) Consider the circuit in Fig. 4. If  $V_{an} = 100 \angle 0^\circ \text{ V}$ ,  $V_{bn} = 60 \angle 60^\circ \text{ V}$ ,  $V_{cn} = 60 \angle 120^\circ \text{ V}$ ,  $X_s = 12 \Omega$ , and  $X_{ab} = X_{bc} = X_{ca} = 5 \Omega$
- (i) Calculate  $I_a$ ,  $I_b$ , and  $I_c$  without using symmetrical components.
- (ii) Calculate  $I_a$ ,  $I_b$ , and  $I_c$  using symmetrical components.

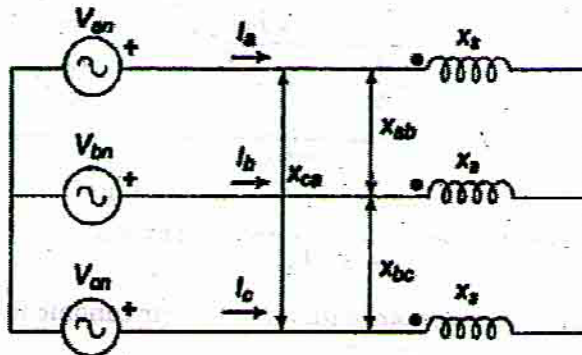


Fig. 4

Or

- (b) Find  $I_1$  and  $I_2$  in the circuit of Fig. 5. Calculate the power absorbed by the  $4\text{-}\Omega$  resistor.

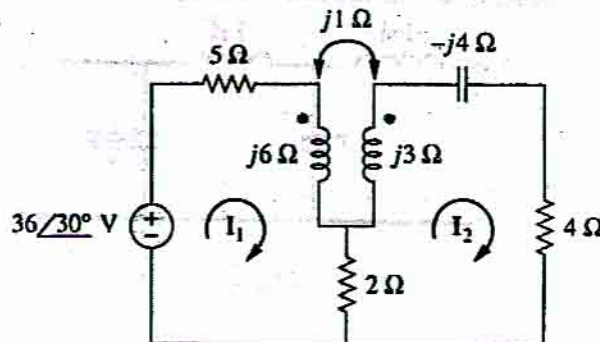


Fig. 5

- III. (a) If  $V_C(0) = 2V$  with the polarities in Fig. 6, write a suitable differential equation and using Laplace transform, find  $V_C(t)$ .

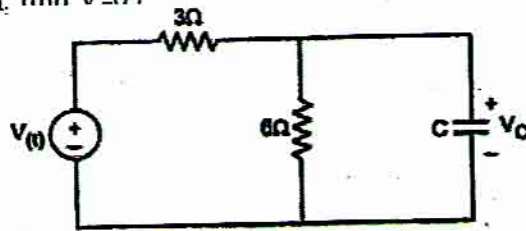


Fig. 6

Or

- (b) For the network function  $V(s) = \frac{5(s+5)}{(s+2)(s+7)}$ , draw pole-zero plot and hence obtain time domain response of voltage.

- IV. (a) The  $z$  parameters of a two port network are  $z_{11} = 20 \Omega$ ,  $z_{22} = 30 \Omega$ ,  $z_{12} = z_{21} = 10 \Omega$ . Find the  $y$  and ABCD parameters of the network.

Or

- (b) Design a T-section and a  $\pi$  section constant  $k$  high pass filter having cut-off frequency of 14 kHz and nominal impedance of  $R_0 = 600 \Omega$ . Also determine (i) its characteristic impedance and phase constant at 26 kHz, and (ii) attenuation at 6 kHz.

- V. (a) Find the Foster Form I and Cauer Form I of the impedance function  $Z(s) = \frac{(s+4)(s+6)}{(s+3)(s+5)}$ , if possible.

Or

- (b) For the circuit in Fig. 7, obtain  $\frac{V_2}{V_s}$ . If  $V_s = \cos \omega t$ , determine  $\omega = \omega_x$  for which the output is real.

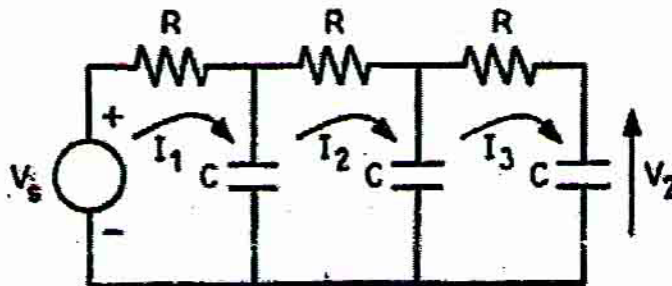


Fig. 7

(4 × 15 = 60 marks)