

C 40960

(Pages : 2)



**FOURTH SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION  
APRIL 2013**

AI 09 403—LINEAR INTEGRATED CIRCUITS AND APPLICATION

(2009 Scheme)

[Regular/Supplementary/Improvement]

Time : Three Hours

Maximum : 70 Marks

**Part A**

*Answer all questions.*

1. What is a planar process ?
2. Define CMRR and slew rate.
3. What is the purpose of current mirror explain ?
4. How zero-crossing detector works ?
5. Design a notch filter for notch frequency of 60 Hz.

(5 × 2 = 10 marks)

**Part B**

*Answer any four questions.*

6. Explain about differential amplifier.
7. Explain the frequency response of op-amp.
8. Explain the operation of V to I convertor.
9. Explain the operation of squarewave generator.
10. Write a note on the switched capacitor filter.
11. Explain the working of timing mark generator.

(4 × 5 = 20 marks)

**Part C**

12. Describe the fabrication of an IC using monolithic technology with suitable figures.


*Or*

13. Discuss the large signal operation of differential amplifier and operation of Ga As amplifier.
14. Analyse the DC and AC characteristic of op-amp in detail.

*Or*

15. Explain the internal circuit of op-amp.

**Turn over**

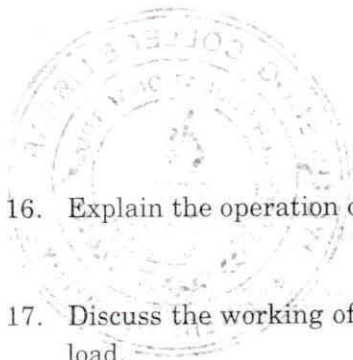

16. Explain the operation of Instrumentation amplifier, Integrator and logarithmic amplifier.

*Or*

17. Discuss the working of precision rectifier, analog multiplier and V to I converter with grounded load.

18. Explain the design steps involved in design of Bandpass filter, universal active filter and Wien bridge oscillator.

*Or*

19. Discuss briefly about Astable multivibrator, sawtooth generator and highpass filter.

(4 × 10 = 40 marks)