

D 70392

(Pages : 3)

Name

Reg

**THIRD SEMESTER B.TECH. (ENGINEERING) (09 SCHEME) DECEMBER EXAMINATION, NOVEMBER 2014**

AI 09 306—ELECTRONIC CIRCUITS AND NETWORK THEORY



Time : Three Hours

Maximum : 70 Marks

**Part A**

*Answer all the questions.  
Each question carries 2 marks.*


1. Define Laplace transform.
2. State the significance of poles and zero of a function.
3. Define characteristic impedance.
4. What is an attenuator ?
5. What are low pass and high pass filters ?

(5 × 2 = 10 marks)

**Part B**

*Answer any four questions.  
Each question carries 5 marks.*

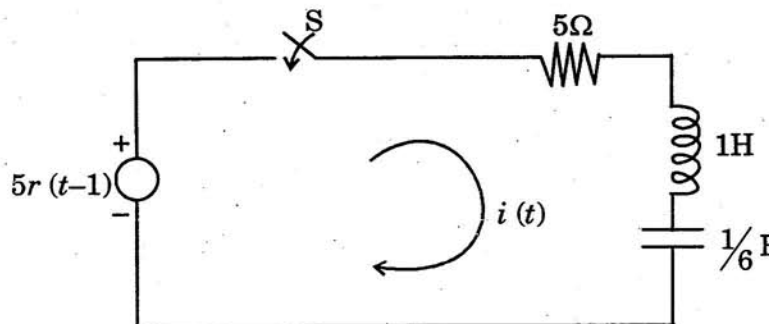6. State and prove any *three* properties of Laplace transform.
7. For the circuit shown below, find the current  $i(t)$  when the switch is closed at  $t = 0$ . Assume that the initial charge on the capacitor is zero.



8. State the restrictions on pole and zero locations in the driving point function.


Turn over

9. Define the various  $z$ -parameters of a two-port network.
10. Design a  $\pi$ -type attenuator to give 20 dB attenuation and to have a characteristic impedance of  $100 \Omega$ .
11. Design a constant  $k$  high pass filter with  $f_c = 4 \text{ kHz}$  and design impedance  $R_0 = 600 \Omega$  (Assume  $\pi$  section).

(4 × 5 = 20 marks)


## Part C

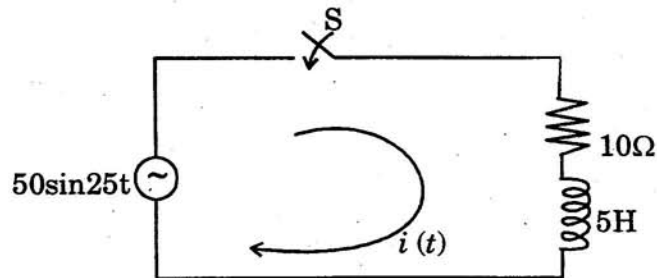12. (a) In the following circuit, a sine wave is applied as input when the switch S is closed at  $t = 0$ . Find the current  $i(t)$




Or

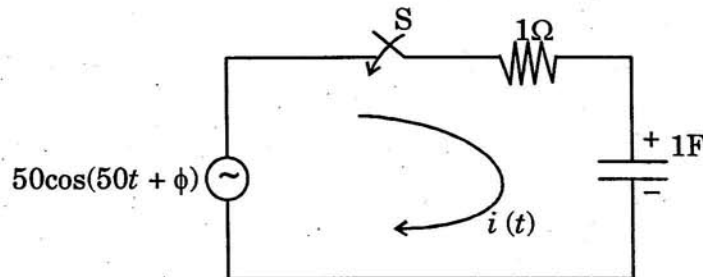- (b) Find the current in the following circuit, when the switch is closed at a time corresponding to  $\phi = 0$ . Assume initial charge on the capacitor is 2 coulombs with polarity shown.



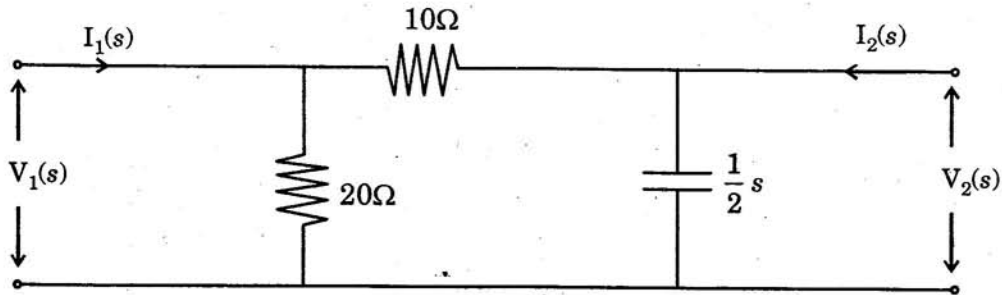13. (a) Find the transfer functions  $G_{21}(s)$ ,  $z_{21}(s)$  and driving point impedance  $z_{11}(s)$  of the following circuit.



Or

- (b) Draw the pole zero diagram for the given network function and hence obtain  $V(t)$

$$V(s) = \frac{4(s+2)s}{(s+1)(s+3)}$$

14. (a) (i) Design a T type attenuator to give an attenuation of 60 dB and to work in a line of 500  $\Omega$  impedance.  
 (ii) Design a symmetrical bridged T-attenuator with an attenuation of 20 dB and terminated into a load of 500  $\Omega$ .

Or

- (b) (i) The impedance parameters of a two port network are  $z_{11} = 6\Omega$ ;  $z_{22} = 4\Omega$ ;  $z_{12} = z_{21} = 3\Omega$ . Find the Y parameters and ABCD parameters and write the describing equations.  
 (ii) Show that each Y parameter of the parallel network is given by the sum of the corresponding parameters of the individual networks.
15. (a) Design a band elimination filter having a design impedance of 600  $\Omega$  and cut-off frequencies  $f_1 = 2\text{kHz}$  and  $f_2 = 6\text{kHz}$ .

Or

- (b) State the characteristics of butterworth and Chebyshev filters.

[4 × 10 = 40 marks]