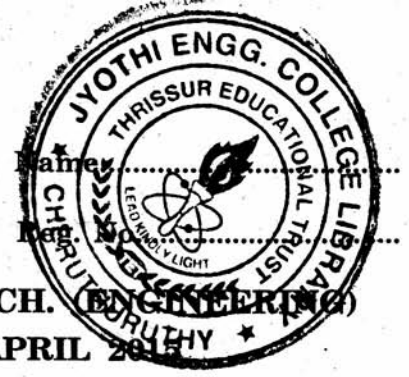


C 80666

(Pages : 4)



**COMBINED FIRST AND SECOND SEMESTER B.TECH. (ENGINEERING)
DEGREE (14 SCHEME) EXAMINATION, APRIL 2015**

**EN 14 107—BASICS OF ELECTRICAL AND ELECTRONICS AND
COMMUNICATION ENGINEERING**

Time : Three Hours

Maximum : 100 Marks

Section 1

PART A

Answer any four questions.

Each question carries 5 marks.

1. Compare the electrical circuit and magnetic circuits. Obtain an expression for MMF. What is its unit.
2. A conductor 30 cm. long rotates about one end at 1000 r.p.m. in a plane perpendicular to a magnetic field of strength 0.5 Wb/m^2 . Find the e.m.f. induced in it.
3. State and explain self inductance and hence to define Coefficient of self inductance.
4. What are the application of a D C Motors.
5. With neat block diagram explain the basic structure of a power system.

(4 × 5 = 20 marks)

PART B

Answer any one question from each module.


Each question carries 15 marks.

MODULE I

6. (a) (i) State and explain Kirchoff's Law. Explain with a neat circuit diagram voltage and current division rule.

Turn over

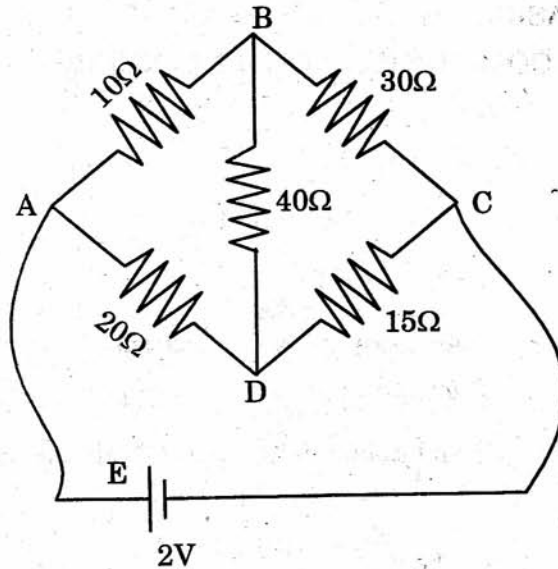- (ii) A bridge network ABCD is arranged as shown in the figure. Determine the value and direction of current in $40\ \Omega$ resistor.



Or

- (b) (i) Explain Phasor diagram of AC. Discuss in detail how it can be used to represent alternating quantities. Explain the theory of a.c. through resistance and inductance in series.
- (ii) A coil having a resistance of $6\ \Omega$ and an inductance of $0.03\ \text{H}$ is connected across $50\ \text{V}$ $60\ \text{Hz}$ supply. Calculate (i) current (ii) phase angle between the current and applied voltage.

MODULE 2

7. (a) (i) With a neat circuit diagram explain the principle and operation of a transformer. What are the different losses in a transformer.
- (ii) A voltage $V = 100 \sin 314 t$ is applied to a circuit consisting of a $25\ \Omega$ resistor and an $80\ \mu\text{F}$ capacitor in series. Determine the p.d. across the capacitor at the instant when the current is one half of its maximum value.

Or

- (b) (i) Discuss the advantages and disadvantages of 3 phase induction motor.
(ii) Explain its principles and working with a neat diagram.

(2 × 15 = 30 marks)

Section 2

PART A

*Answer any four questions.
Each question carries 5 marks.*

1. What do you mean by distortion in amplifiers ?
2. What are different classes of amplifiers ?
3. What is a tank circuit ? Give its function.
4. Draw the block diagram of a AM transmitter and explain function of each block.
5. Discuss the various application of Radar.

(4 × 5 = 20 marks)

PART B

*Answer any one question from each module.
Each question carries 15 marks.*

MODULE 1

6. (a) (i) With help of block diagram of CE amplifier obtain an expression for gain of the amplifier. Discuss its frequency response.
(ii) Give the concept of differential amplifier.

Or

- (b) (i) With help of block diagram explain the principle and operation of a CRO.
(ii) Give the principle of the ADC and DAC.

MODULE 2

7. (a) (i) With help of block diagram explain the principle and operation of superheterodyne radio receiver.

Turn over

- (ii) Explain the principle of RADAR. Write down the RADAR equation and explain its importance.

Or

- (b) (i) With help of block diagram give the principle of satellite communication system. Explain its operation.
- (ii) Briefly explain the advantages of optical communication.

(2 × 15 = 30 marks)