

**C 80700**

(Pages : 2)

Name


Reg. No.

**FOURTH SEMESTER B.TECH. (ENGINEERING) [09 SCHEME] DEGREE  
EXAMINATION, APRIL 2015**

AI 09 403—LINEAR INTEGRATED CIRCUITS AND APPLICATIONS

Time : Three Hours

Maximum : 70 Marks

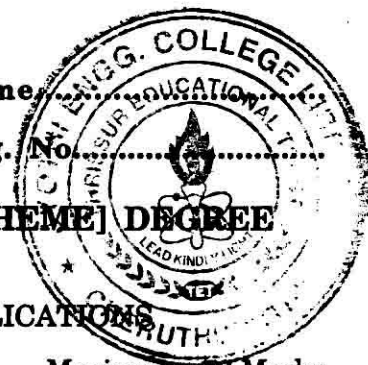

**Part A**

- I. 1 Define CMRR of op-amp.  
2 Define offset voltage of an op-amp.  
3 What is virtual ground ?  
4 Draw the circuit of a voltage follower.  
5 State two advantages of active filter over passive filters.

(5 × 2 = 10 marks)

**Part B**

II. Answer any *four* questions :

- 1 Compare the performance of BJT and FET.  
2 Draw the equivalent circuit of an op-amp and explain.  
3 Derive the expressions for gain of an inverting and non-inverting op-amps.  
4 Explain the working of sample and hold circuits.  
5 Explain the working of switched capacitor integrator.  
6 Explain the principle of an oscillator. State the types of oscillator.

(4 × 5 = 20 marks)

**Part C**

III. 1 Explain the working of BiCMOS amplifier.

*Or*

- 2 Explain the fabrication of BJT.  
3 Discuss the frequency response of an op-amp. Explain a frequency compensation technique.

*Or*

- 4 Draw the internal circuit of 741 op-amp and explain its working.  
5 Explain the working of (i) Instrumentation amplifier ; and (ii) Peak detector.

*Or*

**Turn over**

6 Explain the working of :

- (i) V to I converter with floating fluid.
- (ii) Analog multiplier.

7 Explain the working of a saw-tooth wave generator.

*Or*

8 Derive the transfer function of a second order active Butterworth low-pass filter.

(4 × 10 = 40 marks)