

D 90314

(Pages : 2)

Name.....

Reg. No.....



**SEVENTH SEMESTER B.TECH. (ENGINEERING) DEGREE  
[09 SCHEME] EXAMINATION, NOVEMBER 2015**

**AI 09 704 – ANALOG AND DIGITAL CIRCUIT DESIGN**

Time : Three Hours

Maximum : 70 Marks

**Part A**

*Answer all questions.*

1. Where do sequential statements exist in VHDL?
2. What are the Different object types in VHDL programming?
3. What is Entity?
4. What is MOS Op-Amp?
5. Define Body effect.

(5 × 2 = 10 marks)

**Part B**

*Answer any four questions.*

6. Describe the basic structure of MOSFET.
7. How should a MOSFET be biased so as to operate as a stable current source?
8. Explain briefly about One stage Op-Amps.
9. Explain State Assignment Techniques.
10. Brief about different signal assignment Concurrent structures.
11. Give the VHDL code for Half adder.

(4 × 5 = 20 marks)

**Part C**

*Answer all questions.*

12. (a) Explain in detail about the small signal MOS model.  

*Or*

(b) Explain in detail about the differential pair with MOS leads.
13. (a) Describe in detail about the performance parameters of MOS Op-Amp.  

*Or*

(b) What is a Switched Capacitor Integrator circuit? Explain.

**Turn over**

14. (a) Explain in detail about the sequential statements in VHDL.

Or

(b) Describe the Conversion functions in VHDL.

15. (a) Write VHDL programming for the Multiplexer combinational Circuit.

Or

(b) Write VHDL programming for the Multiplexer sequential Circuit.

(4 × 10 = 40 marks)