

D 90151

(Pages 2)

Name

Reg. No.



**FIFTH SEMESTER B.TECH. (ENGINEERING) [09 SEMESTER DEGREE]
EXAMINATION, NOVEMBER 2015**

EE/PTEE 09 504—POWER ELECTRONICS

Time : Three Hours

Maximum : 70 Marks

Part A

Answer all questions.

1. Why are IGBT becoming popular in their application to controlled converters ?
2. What is the inversion mode of controlled rectifiers ?
3. List various applications of phase controlled converters.
4. What is two quadrant DC chopper ?
5. Define : duty cycle of d.c. chopper.

(5 × 2 = 10 marks)

Part B

Answer any four questions.

6. Explain the principle of operation of DIAC.
7. Explain the turn off characteristics of SCR.
8. For a single-phase Ac voltage controller feeding a R load draw the waveforms of source voltage, output voltage, source and output current.
9. The single-phase half bridge inverter has a resistive load of 2.4Ω and the d.c. input voltage is 48 V. determine the r.m.s output voltage at the fundamental frequency, output power and the total harmonic distortion ?
10. For a type A chopper (first quadrant), express the following variable as a function of V_s , R and duty cycle δ in case the load is resistive.
11. Explain how the switching regulator is differ from linear regulator.

(4 × 5 = 20 marks)

Part C

Answer all questions.

12. (a) Discuss the transfer, output and switching characteristics of IGBT.

Or

- (b) Discuss the operation of power MOSFET and explain the transfer, output and switching characteristics of power MOSFET.

Turn over

13. (a) Discuss the operation of three-phase half controlled rectifier with R load. Also draw the output wave forms.

Or

- (b) Discuss the working of three-phase 180 degree mode operation of inverter with neat sketch and wave forms.
14. (a) Explain with neat diagram and wave forms the four quadrant operation of a chopper with motor load.

Or

- (b) With necessary circuit and waveforms, explain the principle of operation of single-phase to single phase cyclo converter (step up) feeding R load.
15. (a) Draw the circuit diagram of a cuk regulator and explain its operation with equivalent circuit for different modes and waveforms.

Or

- (b) Explain with neat circuit diagram and wave forms the working of pushpull converter.

(4 × 10 = 40 marks)