

D 90005

Name.....

Reg. No.....

**THIRD SEMESTER B.TECH. (ENGINEERING) [14 SCHEME] DEGREE
EXAMINATION, NOVEMBER 2015**

CS/IT 14 305—ELECTRONIC CIRCUITS



Time : Three Hours

Part A

Answer any eight questions.

- I. 1 State the characteristics of a tunnel diode.
- 2 Mention the advantages of using transistors.
- 3 What is an integrator ?
- 4 Bring out the characteristics of E-MOSFET.
- 5 What is ECL ?
- 6 Write about the use of flip-flop.
- 7 Write the characteristics of Read Only Memory.
- 8 When is the magnetic bubble memory used ?
- 9 Mention the working principle of a Schmitt trigger.
- 10 What are the advantages of using depletion mode MOSFET amplifiers ?

(8 × 5 = 40 marks)

Part B

- II. (a) With a neat sketch, explain in detail about working of light-emitting diodes and photo diode.
Or
(b) Discuss in detail about the working mechanism of monostable and astable multi vibrator.
- III. (a) Distinguish between comparators with non-zero references and comparators with hysteresis.
Or
(b) Elaborate in detail about the generation of waveforms using Operational Amplifiers.
- IV. (a) Explain in detail about the working of the CMOS Circuit.
Or
(b) Compare and contrast logic families.
- V. (a) Explain in detail about static and dynamic random access memories.
Or
(b) Discuss in detail about working of A/D and D/A convertors.

(4 × 15 = 60 marks)