

D 90031

(Pages : 3)

Name.....

Reg. No.....

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE [14 SCHEME]
EXAMINATION, NOVEMBER 2015**

EE 14 303—ELECTRIC CIRCUIT THEORY

Time : Three Hours

Maximum : 100 Marks

Part A

Answer any eight questions.


- I. 1 Differentiate the following :—
- Active and passive elements.
 - Dependent and independent elements.
- Explain about series and parallel resonance circuits.
 - Explain the dot convention. Explain how the polarity of voltage is marked in dot convention.
 - With the neat diagram, explain three-phase four wire delta connected system and write down the voltage, power and current equations.
 - Explain the power measurement using two wattmeter methods.
 - Define initial value theorem and final value theorem. Write the equation. Also explain zero sequence positive and negative sequence components.
 - Explain zeros and poles and also describe the pole – zero plot with an example.
 - The z parameters of a two port circuit are $Z_{11} = 1 \text{ k}\Omega$ and $Z_{12} = Z_{21} = Z_{22} = 500 \Omega$. Find the port elements I_1 and I_2 when a 12 V voltage source is connected at the input port and a 250 Ω resistor is connected at the output port.
 - The y -parameter of a two port circuit are $Y_{11} = 5 + j 20 \text{ ms}$, $Y_{12} = y_{21} = -j 20 \text{ ms}$ and $Y_{22} = 0$. Find the input admittance $Y_{in} = I_1 / V_1$ when a 50 Ω resistor is connected at the output port.
 - What is meant by a dependent source ? How many types of dependent sources are there ?

(8 × 5 = 40 marks)

Turn over

Part B

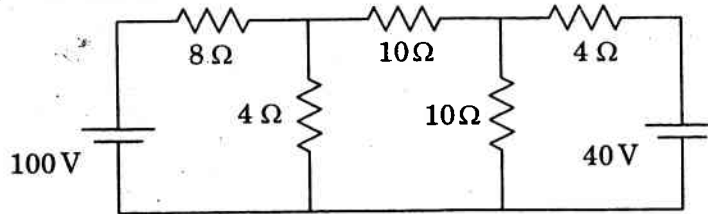- II. (a) Write the mesh equation for the network shown in figure by inspection and find the power absorbed by 8Ω resistor.



Or

- (b) A series circuit has $R = 10 \Omega$, $L = 50 \text{ mh}$ and $C = 100 \mu\text{f}$ and is supplied with 200 V , 50 Hz . Find :


- (i) The impedance.
- (ii) The current.
- (iii) The power.
- (iv) The power factor.
- (v) The voltage drops across each element.

- III. (a) How will you determine the polarity of induced e.m.f. in coupled circuits by dot convention and explain it ?

Or

- (b) For the unbalanced circuit in the figure find :

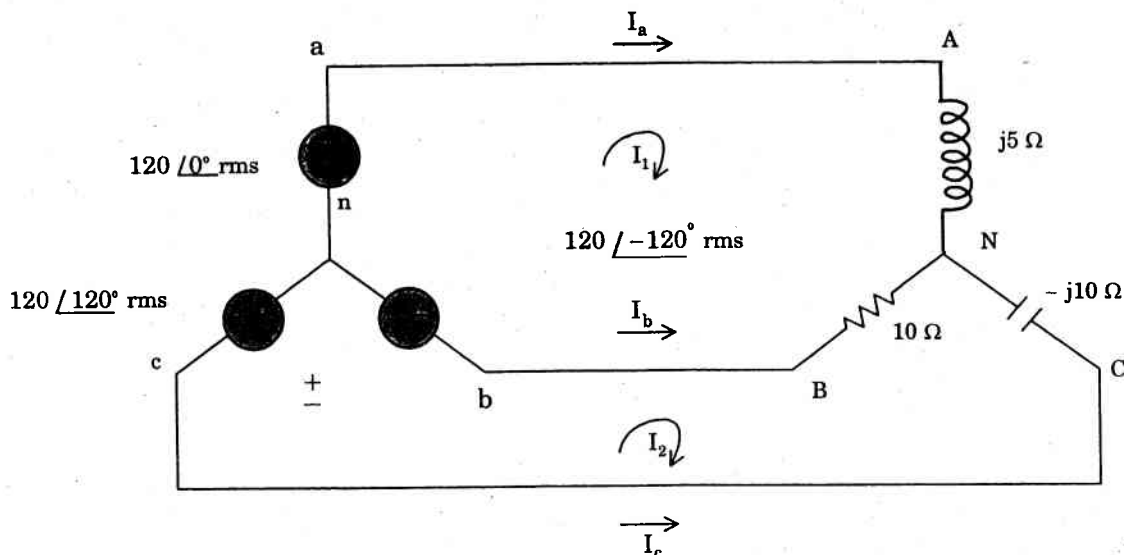
- (i) The line currents.
- (ii) The total complex power absorbed by the load.
- (iii) The total complex power supplied by the source.



- IV. (a) For an RLC series circuit, with a step input, determine the current response $i(t)$ for over damped, critical damped and under damped cases.

Or

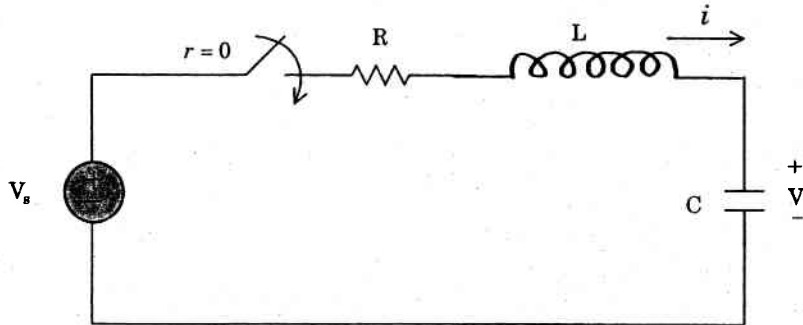- (b) The RLC series circuit of the figure below has $R = 20\Omega$, $L = 0.05\text{ H}$ and $C = 20\ \mu\text{F}$ with 100 V constant source. Find the transient current and assume the switch S is closed at $t = 0$.




- V. (a) Draw the pole-zero plots for the given network function and hence obtain $v(t)$.

$$V(s) = \frac{4(s+2)s}{(s+1)(s+3)}$$

Or

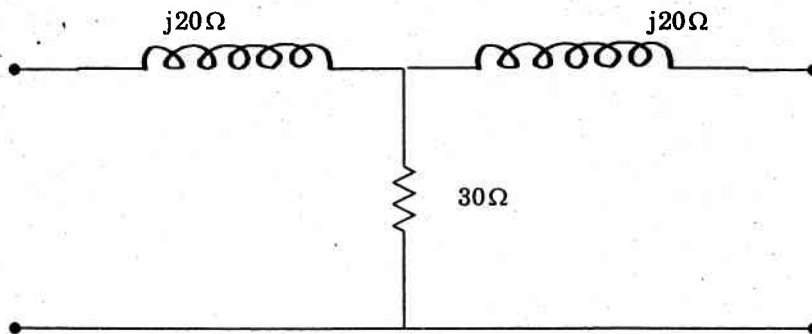- (b) For the network shown in the figure determine Z and Y parameters.



(4 × 15 = 60 marks)