

D 90023

(Pages : 4)

Name.....

Reg. No.....

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE [14 SCHEME]
EXAMINATION, NOVEMBER 2015**

EC 14 303—NETWORK ANALYSIS AND SYNTHESIS



Time : Three Hours

Maximum : 100 Marks


Answer any eight questions.

Part A

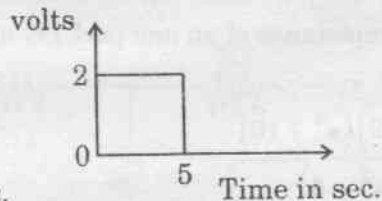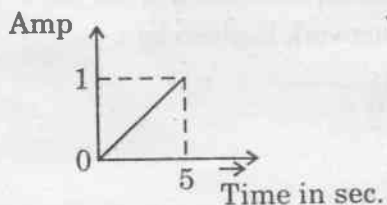
- I. (a) The current and voltage profile of an element Vs time has been shown below. Determine the element and find its value :



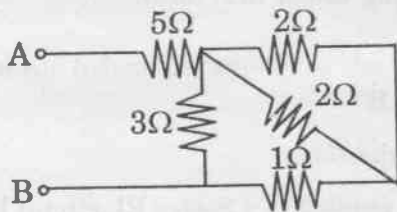- (b) Find the equivalent resistance of the circuit shown across AB.



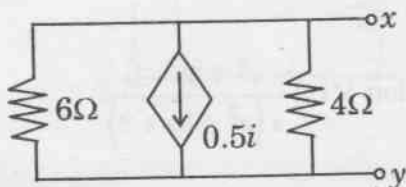- (c) Find Norton's equivalent circuit to the left of the terminal :




- (d) A network function is given by

$$p(s) = \frac{2s}{(s+2)(s^2+2s+s)} \text{ Obtain the pole zero diagram.}$$

Turn over

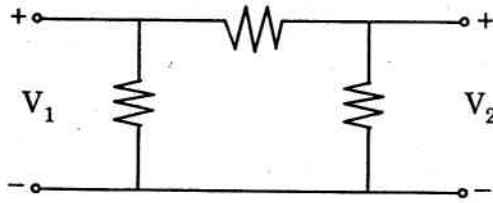- (e) Find the Y parameters of the network shown :



- (f) Explain the characteristics of different types of filter.
- (g) Design a T type attenuator to give an attenuation of 60 dB and to work in a line of 500Ω impedance.
- (h) What is positive real function ? State its properties.
- (i) The driving point impedance of an one port LC network is given by :

$$Z(s) = \frac{2(s^2 + 9)(s^2 + 16)}{s(s^2 + 4)}$$

Obtain the Foster form of LC Network realization.

- (j) How realization of LC network is done using Cauer first form.

(8 × 5 = 40 marks)

Part B

Answer all questions.

- II. (a) (i) A direct voltage of 200 V is suddenly applied to a Series RL circuit having $R = 20 \Omega$ and inductance of 0.2 H. Determine the voltage drop across the inductor at the instant of switching on and at 0.02 sec. later.


(10 marks)

- (ii) Obtain steady state solution of the function $F(s) = \frac{s^2 + 3s + 1}{s(s^2 + 3s + 2)}$.

(5 marks)

Or

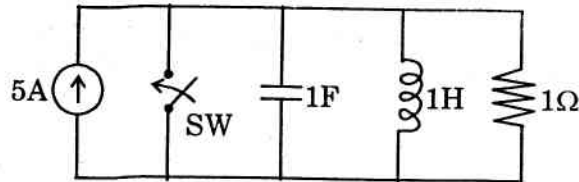- (b) (i) For the figure shown below, find the voltage, across the switch when switch is suddenly opened at $t = 0$. Assume no charge is present on the capacitor and no current is present in the inductor before switching :



(10 marks)


- (ii) State and prove superposition theorem.

(5 marks)

- III. (a) (i) Explain the limitations on pole and zero location in transfer function.

(8 marks)

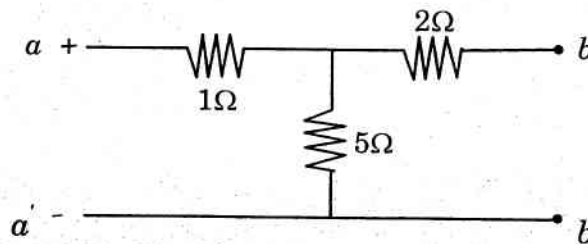
- (ii) Find the transmission parameters for the circuit shown :



(7 marks)

Or

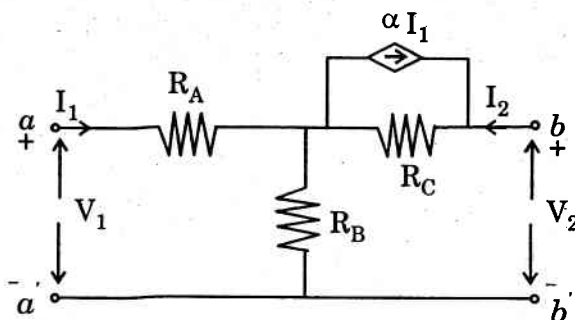- (b) (i) Find the hybrid parameter of the following circuit :—



(8 marks)

- (ii) Obtain the time domain response for the network function $I(s) = \frac{5s}{(s+1)(s^2+4s+8)}$.

(7 marks)

Turn over

- IV. (a) (i) Analyse the design of a third order Low Pass Butterworth filter to meet the specifications $\omega_p = 700$ Hz, $\omega_s = 5000$ Hz, $A_{\max} = 2$ dB, $A_{\min} = 20$ dB.

(8 marks)

- (ii) Analyse and design symmetrical bridged-T attenuator with an attenuation of 20 dB and terminated into a load of 500Ω .

(7 marks)

Or

- (b) (i) Realize Chebyshev's polynomial using approximation. (7 marks)

- (ii) Design a band elimination filter with cut-off frequencies $f_1 = 2$ kHz and $f_2 = 6$ kHz. How transformation from low-pass to High-pass carried out? Give an example.

(8 marks)

- V. (a) (i) Test whether the polynomial

$$p(s) = s^8 + 3s^7 + 10s^6 + 24s^5 + 57s^3 + 50s^2 + 36s + 24 \text{ is Hurwitz.}$$

(5 marks)

- (ii) Synthesize the RL driving point impedance

$$z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

to get Foster first form and Cauer second form of realization.

(10 marks)

Or

- (b) (i) Synthesize the RC driving point impedance $z(s) = \frac{(s+1)(s+3)}{s(s+2)}$ in term of Cauer first and second form of realization.

(10 marks)

- (ii) Check the positive realness of the function $\frac{s^2 + 6s + 5}{s^2 + 9s + 14}$. (5 marks)

[4 × 15 = 60 marks]