

C 1103

(Pages : 2)

Name.....

Reg. No.....

**SIXTH SEMESTER B.TECH. (ENGINEERING) [09 SCHEME] DEGREE
EXAMINATION, APRIL 2016**

EC/PTEC 09 601—VLSI DESIGN



Time : Three Hours

Maximum : 70 Marks

Part A

Answer all the questions

- 1 What are the factors that cause static power dissipation in CMOS circuits ?
- 2 Give the effect of supply voltage and temperature variations on the CMOS system performance.
- 3 Distinguish between depletion mode and enhancement mode MOSFET.
- 4 What is a contrast curve ? Give its significance in VLSI fabrication.
- 5 Define the lambda layout rules.

(5 × 2 = 10 marks)

Part B

Answer any four questions

- 6 Explain different types of technology scaling. Illustrate the impact of full scaling on Drain current, Gate capacitance and power delay product.
- 7 Explain Pseudo NMOS logic.
- 8 Explain the operation of a SRAM with neat sketch.
- 9 Explain Oxidation.
- 10 Explain twin tub process.
- 11 Draw the circuit schematic and stick diagram of CMOS 2 input NAND gate.

(4 × 5 = 20 marks)

Part C

Answer all questions

- 12 (a) Explain the operation of a CMOS inverter and derive an expression for its propagation delay.
- Or*
- (b) Explain the transfer plot of CMOS inverter with necessary expression for V_{out} in each region.

Turn over

13 (a) How to read or write and hold the bit in SRAM cell ?

Or

(b) Explain the working of 1-transistor DRAM cell. Give the difference between SRAM and DRAM.

14 (a) What is Oxide masking ? Explain how impurity redistribution takes place during oxide growth.

Or

(b) Explain the constant source diffusion and the limited source diffusion process.

15 (a) Explain LOCOS, SILO and SWAMI process.

Or

(b) Describe in detail step-by-step procedure of P-well CMOS fabrication.

(4 × 10 = 40 marks)