

D 12047


(Pages : 2)

Name.....

Reg. No.....

**FIFTH SEMESTER B.TECH. (ENGINEERING) [14 SCHEME] DEGREE
EXAMINATION, NOVEMBER 2016**

EE 14 501—POWER ELECTRONICS

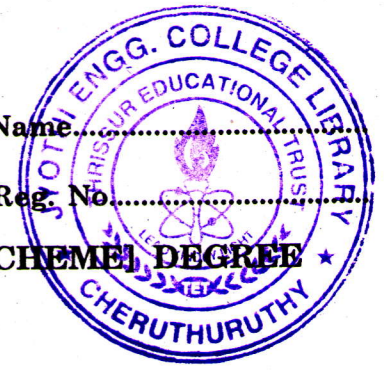

Time : Three Hours

Maximum : 100 Marks

Part A

Answer all eight questions.

- I. (a) Explain the effect of gating current on VI characteristics of an SCR.
- (b) Describe R triggering for a thyristor gate drive in detail.
- (c) Discuss the operation of freewheeling diodes in a controlled rectifier?
- (d) Compare the dual converter with and without circulating current.
- (e) Draw a neat sketch of PWM inverter. Explain its principle in detail.
- (f) What is meant by positive and negative converter group in a cyclo converter? and write its application.
- (g) Compare class-A and B chopper.
- (h) Distinguish the SMPS and SMPC.
- (i) Explain the class - F commutation circuit for SCR.
- (j) Draw and explain the reverse recovery characteristics of a power diode.

(8 × 5 = 40 marks)

Part B

Answer all questions.

- II. (a) Explain the construction, operation and switching characteristics of BJT. (15 marks)

Or

- (b) Draw and explain the forward characteristics of SCR using *two* transistor model of SCR. (15 marks)

- III. (a) With a circuit and waveform explain three phase half controlled rectifier with RL load for $\alpha = 120^\circ$. (15 marks)

Or

- (b) Explain the operation of single phase dual converter with circulating and non circulating current type. (15 marks)

(15 marks)

Turn over

IV (a) What is Pulse Width Modulation ? Discuss any *two* of its techniques with neat diagrams.

(15 marks)

Or

(b) Discuss the working of a single phase cycloconverter with its circuit and waveform.

(15 marks)

V. (a) A step down d.c. chopper has input voltage of 230 V with 10Ω load, voltage drop across chopper is 2V, when it is on. For a duty cycle of 0.5. Calculate (i) Average and r.m.s. value of output voltage ; and (ii) Power delivered to the load.

(15 marks)

Or

(b) Discuss the different configurations of UPS and explain them in detail. (15 marks)

[4 × 15 = 60 marks]