

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY  
THIRD SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2017

Course Code: CS207

Course Name: ELECTRONIC DEVICES AND CIRCUITS (CS)


Max. Marks: 100

Duration: 3 Hours

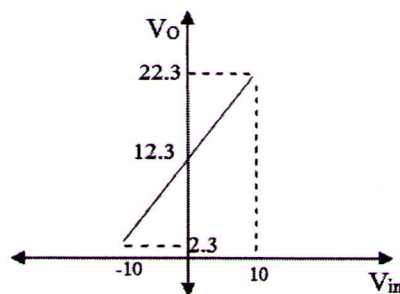
**PART A***Answer all questions, each carries 3 marks.*

Marks

- 1 Design a clamper circuit to get the following transfer characteristics, assuming voltage drop across the diode is 0.7V. (3)



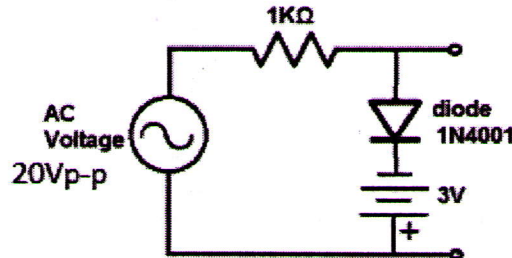- 2 Draw the output waveform of the following circuit, assuming voltage drop across the diode is 0.7V. (3)



- 3 Compare linear regulator with switching regulator. (3)  
4 Compare FET with BJT (3)

**PART B***Answer any two full questions, each carries 9 marks.*

- 5 a) With neat sketches explain the principle and working of RC integrator circuit. (5)  
b) Explain the response of an RC integrator circuit for a square wave input. (4)  
6 a) With neat sketches explain the working of n-channel JFET. (5)  
b) Draw the characteristics of n-channel JFET (4)  
7 a) Draw and explain a circuit whose output voltage is three times as that of input voltage. (5)  
b) Discuss about simple zener shunt voltage regulator with the help of circuit diagram. (4)

**PART C***Answer all questions, each carries 3 marks.*

- 8 Define stability factor. Write down the expression for stability factor S. (3)  
9 Compare positive feedback with negative feedback. (3)

- 10 What is meant by sustained oscillation? What are the criteria's for obtaining sustained oscillations? (3)
- 11 An astable multivibrator having  $R_1 = 2K\Omega$ ,  $R_2 = 20K\Omega$  and  $C_1 = 0.01\mu F$ ,  $C_2 = 0.05\mu F$ . Determine the period and frequency of oscillation. (3)

### PART D


*Answer any two full questions, each carries 9 marks.*

- 12 a) With the help of circuit diagram explain the working of RC coupled amplifier. (5)  
b) Draw and explain the frequency response of RC coupled amplifier. (4)
- 13 a) With neat diagram explain the working of Hartley oscillator using BJT. (4)  
b) Derive the expression for frequency of oscillation and loop gain of a Hartley oscillator using BJT. (5)
- 14 a) Explain the effect of negative feedback on amplifiers. (5)  
b) With neat diagram explain the working of monostable multivibrator using BJT (4)
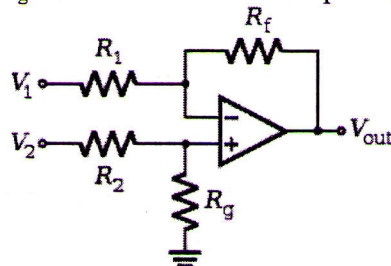
### PART E

*Answer any four full questions, each carries 10 marks.*

- 15 a) With neat diagram explain the working and hysteresis curve of a non inverting Schmitt trigger using op amp. (6)  
b) The difference amplifier shown in the figure having  $R_1 = R_2 = 5K\Omega$ ,  $R_F = 10K\Omega$ ,  $R_g = 1k\Omega$ . Calculate the output voltage. (4)



- 16 a) Explain RC differentiator circuit using op amp. (4)  
b) With the help of diagram explain a three input inverting summing amplifier. (4)  
c) Realize a circuit to obtain  $V_o = -2V_1 + 3V_2 + 4V_3$  using operational amplifier. Use minimum value of resistance as  $10K\Omega$ . (2)
- 17 a) With neat diagram explain the working of wien bridge oscillator using op-amp. (5)  
b) Derive the expression for frequency of oscillation of Wien bridge oscillator using op-amp. (5)
- 18 a) Explain the working principle of a successive approximation type ADC. (5)  
b) A 4-bit R-2R ladder type DAC having  $R = 10 K\Omega$  and  $V_R = 10V$ . Find its resolution and output voltage for an input 1101. (5)
- 19 a) Draw the circuit diagram and frequency response of a second order high pass butterworth filter using OP-AMP and explain its working. (5)  
b) Design a first order butterworth LPF using OP-AMP for a high cut of frequency of 1KHz and passband gain is 2. Give the design steps and draw the frequency response. (Assume  $C = 0.01\mu F$ ) (5)
- 20 a) With neat diagram explain the working of IC555 timer. (5)  
b) Design an astable multivibrator using IC 555 timer for a frequency of 1KHz and a duty cycle of 70%. Assume  $c = 0.1\mu F$ . (5)

\*\*\*\*