

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
THIRD SEMESTER B.TECH DEGREE EXAMINATION, APRIL 2018

Course Code: EE203

Course Name: ANALOG ELECTRONIC CIRCUITS (EE)

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 5 marks

Marks

- 1 (a) Design a suitable circuit to obtain the output level clipped at +3V and -4V for a 10V peak to peak sinusoidal input voltage. (3)
- (b) What are the factors affecting stability of operating point of a transistor? (2)
- 2 Draw and explain high frequency hybrid pi model of common emitter transistor. (5)
- 3 What are the different topologies of feedback amplifiers? (5)
- 4 (a) What are the properties of an ideal opamp? (3)
- (b) State Barkhausen criteria for sinusoidal oscillators. (2)
- 5 With the help of a circuit diagram show how an opamp is used to get an output as $V_o = V_1 + V_2 - V_3 - V_4$, Where V_1, V_2, V_3 and V_4 are inputs to opamp. (5)
- 6 Design an integrator that can integrate a square wave of peak to peak voltage 10V and frequency 1 kHz and draw the output waveform. (5)
- 7 Explain the operation of a square waveform generator using opamp. (5)
- 8 Design a Wein bridge oscillator to generate a sinusoidal waveform of 1 kHz. (5)

PART B

Answer any two full questions, each carries 10 marks

- 9 (a) Design a voltage divider bias circuit for a NPN transistor with $h_{fe} = 100$ and $V_{BE} = 0.6$ V, to operate from a 12 V dc supply. The bias conditions are $V_{CE} = 6$ V, $V_E = 1.2$ V and $I_C = 2$ mA. (5)
- (b) Explain any one compensation technique used for reducing the drift of operating point. (5)
- 10 (a) Draw the h parameter model of a transistor in CE configuration. Also derive the expression for input impedance, current gain and voltage gain. (5)
- (b) h-parameters of a transistor connected in CE configuration is $h_{ie} = 1000 \Omega$, $h_{re} = 10 \times 10^{-4}$; $h_{fe} = 50$; $h_{oe} = 100 \times 10^{-6} \Omega$. If the load resistance R_L is 1 K Ω , find:
i) The input impedance ii) Current gain iii) Voltage gain (5)
- 11 (a) Explain the working and characteristics of a N channel MOSFET. (6)
- (b) Draw the frequency response of an amplifier. What is the significance of gain bandwidth product? (4)

PART C

Answer any two full questions, each carries 10 marks

- 12 (a) What is harmonics distortion in power amplifier? Discuss the operation of a class (6)

- B power amplifier and derive its maximum power conversion efficiency.
- 13 (b) Explain the working of a two stage RC coupled amplifier with circuit diagram. (4)
- (a) Derive the expression for the voltage gain of an opamp based non-inverting amplifier. (5)
- (b) Derive the frequency of oscillation of a RC phase shift oscillator using transistor. (5)
- 14 (a) Write short notes on the following: (4)
- i) CMRR ii) Slew rate
- (b) Explain the operation of Hartley oscillator with a circuit diagram. (6)

PART D

Answer any two full questions, each carries 10 marks

- 15 (a) Draw and explain the operation of logarithmic amplifier. (5)
- (b) What is the significance of UTP and LTP in Schmitt trigger circuits? Why is it called as regenerative comparator? (5)
- 16 (a) What are the features of instrumentation amplifier? Derive the expression for output voltage of an instrumentation amplifier. (5)
- (b) Draw and explain the operation of a Triangular waveform generator using opamp (5)
- 17 (a) With the help of internal circuit diagram of IC555 explain the operation of a monostable multivibrator. (5)
- (b) Design an astable multivibrator using 555 timer to generate an output signal with frequency 5kHz and 50% duty cycle. (5)
