

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
THIRD SEMESTER B.TECH DEGREE EXAMINATION, DECEMBER 2018

Course Code: EE209

Course Name: ELECTRICAL TECHNOLOGY (MC)

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 5 marks.


	Marks
1 Explain in detail about delta to star conversion.	(5)
2 Define super position theorem and write its steps to solve the problems.	(5)
3 Define resonant circuit. Derive the expression for find resonance frequency of RLC series circuit.	(5)
4 Derive EMF equation of DC Generator.	(5)
5 Explain in shortly about transformer losses.	(5)
6 Sketch and explain Torque-Slip characteristics of 3 phase induction motor.	(5)
7 Explain shortly about stepper motor and its types.	(5)
8 Write the types of single phase induction motors and its applications	(5)

PART B

Answer any three full questions, each carries 10 marks.

9

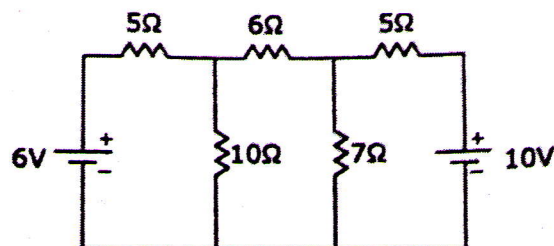
Find the node voltage V_1 and V_2 using nodal analysis for the given circuit.



(10)

10 Find I_3 through mesh analysis for the following figure.

(10)

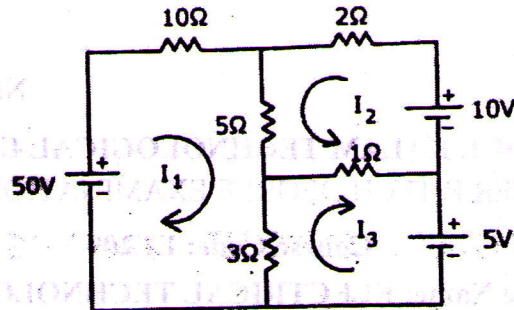

- 11 State maximum power transfer theorem. Obtain the condition for maximum power transfer. (10)
- 12 Explain in detail about three phase power measurement using wattmeter with neat diagram. (10)
- 13 Derive the torque equation of DC motor. (10)

PART C

Answer any two full questions, each carries 15 marks.

- 14 What are the necessities of starter? Explain with sketch any three starting method of three phase induction motor. (15)
- 15 Derive the torque equation, condition for maximum running torque, starting and full load torque of three phase induction motor (15)
- 16 Explain principle, construction and working of single phase induction motor with its neat sketch. (15)
- 17 Explain the working concept of synchronous motor with its advantages, disadvantages and applications. (15)

