

Answer all six questions.

Modules 1 to 6: Part 'a' of each question is compulsory and answer either part 'b' or part 'c' of each question.

Q.no.	Module 1	Marks
1.a	Obtain the relation for average output current for a dc-dc boost converter at the boundary between continuous and discontinuous mode of operation	3
	Answer b or c	
b	With the help of relevant waveforms, derive the following for a dc-dc buck converter (i) input-output voltage relation in terms of duty ratio for continuous conduction mode (ii) output voltage ripple	6
c	Explain the working of a basic forward converter. Explain the role of demagnetizing winding in tackling the issue of stored energy due to transformer magnetizing current and avoiding the chances of converter failure.	6
Q.no.	Module 2	Marks
2.a	With the help of circuit diagram and relevant waveforms, discuss the working principle of half bridge converter	3
	Answer b or c	
b	With the help of circuit diagram and relevant waveforms, discuss the working principle of Full bridge converter	6
c	Explain the voltage mode control principle of a Flyback converter	6
Q.no.	Module 3	Marks
3.a	What are the various criteria for the stable loop operation for a typical converter with feedback	3

Answer b or c



- b Explain the shaping of gain versus frequency characteristic of converter for stable operation 6
- c Explain the technical reasons for the advantages of current mode control of converter over voltage mode control. Also, List the disadvantages of it. 6

Q.no.	Module 4	Marks
4.a	What is meant by state space averaging? What are the basic steps in obtaining it for a converter?	3

Answer b or c

- b Discuss and derive the small signal model for any one basic switched mode dc-dc converter 6
- c Obtain the small signal ac equivalent circuit model for a non-ideal flyback converter with help of relevant equations and sketches. Take the main switch internal resistance as R_{on} . 6

Q.no.	Module 5	Marks
5.a	Explain the purpose and concept of average switch modelling?	4

Answer b or c

- b Derive the state space averaging model of non-ideal buck boost converter 8
- c Explain in detail modelling of pulse width modulator. 8

Q.no.	Module 6	Marks
6.a	What is meant by resonant converters? How are they useful in smpc applications?	4

Answer b or c

- b With the help of neat circuit diagram and relevant waveforms, discuss the operation of series loaded resonant dc-dc converter in discontinuous current conduction mode. 8
- c Explain the working of ZVS resonant switch converter with neat sketches. 8