 


Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_



**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
**FIFTH SEMESTER B.TECH DEGREE EXAMINATION(R&S), DECEMBER 2019**

**Course Code: EC361**

**Course Name: DIGITAL SYSTEM DESIGN**

Max. Marks: 100


Duration: 3 Hours

**PART A**

*Answer any two full questions, each carries 15 marks.*

Marks

 - 1 a) Study the CSSN shown below and obtain the excitation expressions, excitation/ state transition table, state table and state diagram. (9)




- b) Generate an ASM chart for a Mealy network that detects non-overlapping sequence of 101. (6)
- 2 a) Find the reduced flow table from the primitive flow table of a fundamental mode asynchronous sequential circuit given below. (9)

Present State	Next state				Output			
	x=00	x=01	x=10	x=11	x=00	x=01	x=10	x=11
a	c	a	b	-	-	0	-	-
b	-	a	b	e	-	-	1	-
c	c	a	-	d	0	-	-	-
d	c	-	b	d	-	-	-	0
e	f	-	b	e	-	-	-	1
f	f	-	-	e	1	-	-	-

- b) Explain critical and non-critical races in asynchronous sequential circuits with the aid of an appropriate state transition table. (6)
- 3 a) Examine the ASC shown below to generate the excitation/transition table, state (7.5)

table, flow table and flow diagram.

 

- b) Using implication charts, construct a minimal state table from the state table given (7.5) below.


Present State	Next State		Output
	X=0	X=1	
A	B	C	1
B	D	E	0
C	A	F	0
D	E	C	0
E	G	H	1
F	B	H	1
G	D	F	0
H	F	E	1

**PART B**

Answer any two full questions, each carries 15 marks.


- 4 a) Draw the logic circuit diagram of the SOP expression  $f = \sum(2,3,6,7,11,12,13,15)$ . (7.5)  
 Examine the possibility of hazards in the circuit. Explain how the hazard can be detected and eliminated with the aid of Karnaugh map.
- b) Explain essential hazards in asynchronous sequential circuits. (7.5)
- 5 a) For the circuit given in figure below, find the test vectors for the following faults (7.5)  
 using path sensitization.

 - (i) SA0 at  $x_3$  (ii) SA1 at  $x_3$  (iii) SA0 at g (iv) SA1 at g.



 - b) Construct a table listing the set of all possible single stuck-at faults and the faulty (7.5)

and fault-free responses of the circuit shown below. Also find the fault cover table and identify the minimal complete test set.



- 6 a) Describe the operation of data synchronizers with the help of suitable timing diagrams. (7.5)
- b) Find the test vectors for all SA0 and SA1 faults in the circuit whose Boolean function is  $f = x_1x_2 + x_2'x_3 + x_3x_4'$  using Kohavi algorithm. (7.5)

### PART C

*Answer any two full questions, each carries 20 marks.*

- 7 a) Explain PLA folding. Define foldable compatibility matrix and state its properties. (12)
- b) Determine the minimal test set for PLA  $f = x_1x_2 + x_2x_4 + x_1x_3'x_4'$  (8)
- 8 a) Describe the simplified block diagram of configurable logic block of XC4000 FPGA family. (10)
- b) Explain the switch matrix of Xilinx 9500 CPLD family with the help of a diagram. (10)
- 9 a) Explain various test generation techniques of PLA. (10)
- b) With a suitable diagram, describe the input-output block architecture of Xilinx 9500 CPLD family. (10)

\*\*\*\*