

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third semester B.Tech examinations (S) September 2020

Course Code: EC209**Course Name: ANALOG ELECTRONICS (MC)**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer all questions, each carries 5 marks.*

Marks

- | | | |
|---|----------------------------------------------------------------|-----|
| 1 | Elucidate about piece wise linear model of diode. | (5) |
| 2 | Give a brief idea about the load line concept in BJT. | (5) |
| 3 | Explain the operation of JFET with a neat sketch. | (5) |
| 4 | With a neat sketch, explain Darlington pair of transistors. | (5) |
| 5 | Describe the classification of oscillators with examples. | (5) |
| 6 | Derive the frequency of oscillation of Colpitts oscillator. | (5) |
| 7 | With a neat block diagram explain the working of SMPS circuit. | (5) |
| 8 | Explain the operation of Phase Locked Loop. | (5) |

PART B*Answer any three questions, each carries 10 marks.*

- | | | |
|----|--------------------------------------------------------------------------------------------------------------------------------------------|------|
| 9 | a) Explain how Zener diode acts as a voltage regulator. | (5) |
| | b) Draw the circuit diagrams and corresponding waveforms of a positive clipper with positive bias and positive clipper with negative bias. | (5) |
| 10 | Draw the h-parameter model of a CE amplifier and derive the expression for voltage gain, current gain, input and output impedance. | (10) |
| 11 | Explain the working of a common source amplifier with a neat sketch. | (10) |
| 12 | Elaborate the operation of class A power amplifier and derive its efficiency. | (10) |
| 13 | Explain E-MOSFET and D-MOSFET with relevant diagrams. | (10) |

PART C*Answer any two questions, each carries 15 marks.*

- | | | |
|----|-------------------------------------------------------------------------------------------------------|------|
| 14 | Explain RC phase shift oscillator using BJT and derive its frequency of oscillation. | (15) |
| 15 | a) Explain the operation of astable mode of operation of multivibrators using BJT with a neat sketch. | (10) |
| | b) Derive an equation for frequency of oscillation of Hartley oscillator. | (5) |

- 16 a) Draw the internal circuitry of IC555 in monostable mode and explain its working. (10)
- b) Explain any one application of PLL. (5)
- 17 a) Explain the construction and characteristics of UJT. (10)
- b) Illustrate about online UPS and offline UPS. (5)
