

**C 58196**

Name.....

Reg. No.....

**FOURTH SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION  
JUNE 2009**

**CS 04 406—ELECTRONIC CIRCUITS AND SYSTEMS**

(2004 admissions)

Time : Three Hours

Maximum : 100 Marks

**Part A**

*Answer all questions.*

1. What is a clipper ? Explain briefly.
2. Need for bootstrap sweep generator.
3. Distinguish different logic levels.
4. Explain the concept of SSI and MSI and differentiate them.
5. What is programmable ROM ? Explain briefly.
6. What is memory expansion ?
7. Distinguish External and Internal noise.
8. Briefly explain FM demodulation.

(8 × 5 = 40 marks)

**Part B**

1. Draw the clamping circuits and explain in detail with help of waveforms.

*Or*

Explain Bistable multivibrator with a help of a neat sketch.

(15 marks)

2. Explain the concepts of SSI, MSI, LSI and VLSI. Differentiate them and explain in detail.

*Or*

Explain TTL flip-flops in detail with neat sketch.

(15 marks)

3. Explain about the different classifications made in ROM.

*Or*

Explain DAC and ADC in detail with neat sketch.

(15 marks)

4. Explain frequency and phase modulation in detail.

*Or*

Explain in detail about the radiation and propagation of EM waves.

(15 marks)

[4 × 15 = 60 marks]