

C 58202

(Pages 2)

Name.....

Reg. No.....

**FOURTH SEMESTER B.TECH. (ENGINEERING) DEGREE
EXAMINATION, JUNE 2009**

AI/BM 04 406—LINEAR INTEGRATED CIRCUITS AND APPLICATIONS

(2004 Admissions)

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

- I. (a) What is photolithography ? Explain.
(b) Differentiate Thin film technology from Thick film technology.
(c) Draw the block diagram of an op-amp. Explain it.
(d) Define Slew rate. Explain its significance.
(e) Draw an op-amp inverter. Obtain its output voltage.
(f) Draw op-amp zero crossing detector and explain its principle.
(g) State and explain Barkhausen criterion for oscillation.
(h) Draw op-amp all pass filter and explain.
- (8 × 5 = 40 marks)
- II. (a) Explain the fabrication of BJTs using CMOS technology with neat sketches.
Or
(b) Broadly differentiate monolithic IC technology from hybrid IC technology.
- III. (a) Draw the equivalent circuit of an op-amp. Derive an expression for output voltage.
Or
(b) (i) Explain the causes of slew rate.
(ii) Draw 741 op-amp simplified internal circuit and explain.
- IV. (a) Explain the following op-amp circuits with neat sketches :—
(i) Op-amp log amplifier.
(ii) Op-amp peak detector.

Or

Turn over

- (b) Draw op-amp integrator and differentiator and explain their operation. Derive expressions for output voltages.
- V. (a) Draw op-amp Wien bridge oscillator and explain its principle. Derive the condition for oscillation.

Or

- (b) (i) Explain the theory of operation of switched capacitor filter.
- (ii) Explain the principle of op-amp bistable multivibrator with a neat diagram.

(4 × 15 = 60 marks)