

EE  
C 46683

Name .....

Reg. No. ....



**EIGHTH SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION  
JUNE 2008**

**EE 04 802—INDUSTRIAL DRIVES**

**(2004 Admissions)**

**Time : Three Hours**

**Maximum : 100 Marks**

*Answer all questions.*

- I. (a) Explain the block diagram of a typical electric drive.  
(b) What are the three types of d.c. drives based on their input supply?  
(c) What is two-quadrant d.c. drive?  
(d) Write a note on solar powered drives.  
(e) Where step up chopper is used?  
(f) Explain the concept of V/f control.  
(g) How brushless d.c. motor drives work?  
(h) What are the characteristics of varistors?  

(8 × 5 = 40 marks)
2. (a) Give the open loop block diagram of separately excited d.c. motor drive. Explain the block diagram and derive the important parameters involved.  

Or

- (b) Give the schematic for the PLL control of electric drives and explain the principle involved.
3. (a) Draw the circuit of a single-phase dual converter d.c. drive and discuss the operation. What are the performance parameters? How they are assessed?  

Or

- (b) Write a detailed note on braking of d.c. motors using rectifiers and choppers.
4. (a) With suitable diagrams, explain the principle of VSI fed induction motor drive. Discuss the features.  

Or

- (b) Give the schematic of a PWM drive. What are the advantages of PWM?
5. (a) With schematic diagram and flow charts, explain the principle of Microprocessor control of D.C. and A.C. drives.  

Or

- (b) With necessary derivations, obtain steady state torque-load angle characteristics of salient pole synchronous machine.

(1 × 15 = 60 marks)