

C 47607

(Pages : 2)

Name.....

Reg. No.....

**SIXTH SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION
JUNE 2008**

EC 04 605—POWER ELECTRONICS

(2004 admissions)

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

- I. (a) Differentiate MOSFET from IGBT.
(b) Explain the static and dynamic characteristics of thyristor.
(c) Draw a neat diagram of single-phase rectifier with 'RL' loads and explain.
(d) Draw a neat circuit diagram of bridge inverter and explain its principle in detail.
(e) Explain in detail the principle of operation of step-up chopper with a neat sketch.
(f) What are the methods to control the speed of D.C. motors ? Explain any one method in detail with a neat sketch.
(g) Differentiate switching Regulator from ordinary Voltage Regulator.
(h) Draw a neat block diagram of an UPS and explain.
- (8 × 5 = 40 marks)
- II. (a) (i) Explain the basic structure and V-I characteristics of power diodes with neat diagrams. (7 marks)
(ii) Give an account on gate triggering circuit using UJT. (8 marks)
- Or*
- (b) (i) Explain the construction and V-I characteristics of TRIAC with neat sketches. (7 marks)
(ii) Differentiate power transistor from power diodes. (8 marks)
- I. (a) (i) Draw a single-phase rectifier using SCR with RL loads and explain its principle in detail. (7 marks)
(ii) Differentiate Converter from Inverter. (8 marks)
- Or*
- (b) (i) Draw a neat circuit diagram of pulse width modulated inverter and explain its operation in detail. (7 marks)
(ii) Explain in brief "the principle of SCR Inverters". (8 marks)

Turn over

- IV. (a) (i) Explain the requirement for an Ideal a.c. regulator. (7 marks)
(ii) Draw a neat circuit diagram of a simple cyclo converter. Explain its principle of operation. (8 marks)

Or

- (b) Write short notes on :
(i) Speed control of D.C motors. (7 marks)
(ii) Step-down choppers. (8 marks)

- V. (a) Draw a neat block diagram of SMPS. Explain its principle of operation. Enumerate its features and applications.

Or

- (b) (i) Compare the parameters of linear mode power supply from switched mode power supply. (7 marks)
(ii) Explain the design steps with equation of an UPS. (8 marks)

[4 × 15 = 60 marks]