

D 51223

(Pages : 2)

Name.....

Reg. No.....

**COMBINED FIRST AND SECOND SEMESTER B.TECH. (ENGINEERING)
DEGREE EXAMINATION, DECEMBER 2008**

CS/IT/PT 2K 109—BASIC ELECTRICAL ENGINEERING

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

- I. (a) Write Kirchhoff's current and voltage laws.
- (b) Give the units of force, energy and flux density.
- (c) Explain the term series resonance.
- (d) Write short notes on forced response.
- (e) Write the principle of energy meter.
- (f) What is meant by regulation ? Explain.
- (g) Write the concept of d.c. motor.
- (h) Draw the circuit model of an alternator and explain.

(8 × 5 = 40 marks)

- II. (a) Find the current in the 2-ohm resistor of Fig. 1 by the principle of superposition.

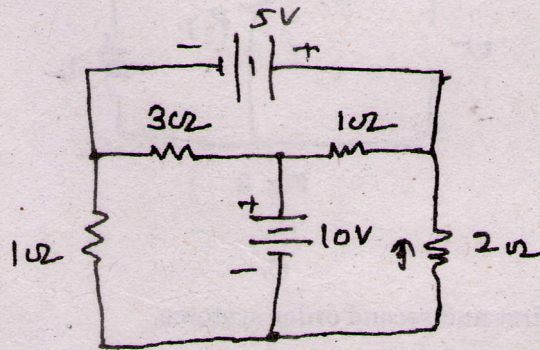


Fig. 1

(15 marks)

Or

Turn over

- (b) Find the Thevenin's and Norton's equivalent circuit at terminals a-b for the network of Fig. 2

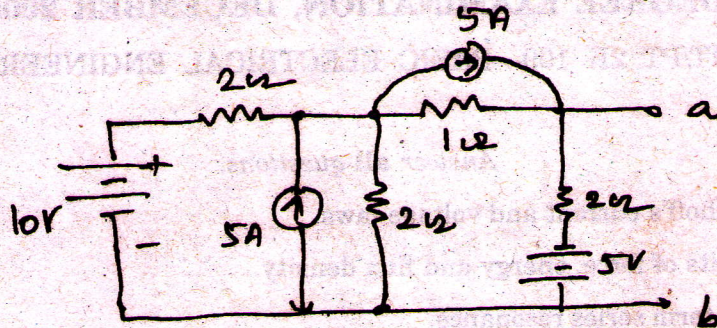


Fig. 2

(15 marks)

- III. (a) In the circuit, given in Fig. 3 $R_1 = 2 \Omega$, $R_2 = 6 \Omega$ and $L = 3 \text{ H}$.

- Find the enough points to plot $Z(s)$.
- What is the impedance of this circuit to direct current?
- If a voltage $v = V_0 e^{st}$ is acting where $V_0 = 1\text{V}$, what current i flows for $s = -4$?



Fig. 3

(15 marks)

Or

- (b) Give examples for first and second order systems. (15 marks)
- IV. (a) (i) Discuss the transformer in detail. (7 marks)
- (ii) Write the principle of electromagnetics. (8 marks)

Or

- (b) Discuss the principle of moving iron instruments. (15 marks)
- V. (a) Explain the principle of D.C. generator. (15 marks)

Or

- (b) Explain the basic principle of operation of induction motor. (15 marks)

[4 × 15 = 60 marks]