

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE
EXAMINATION, DECEMBER 2008**

EC/AI 04 403—ELECTRIC CIRCUIT AND NETWORK THEORY

(2004 Admissions)

Time : Three Hours

Maximum : 100 Marks

Part A

Answer all the questions.

- I. Find $V(s)$ for the given waveform in Fig. 1. :

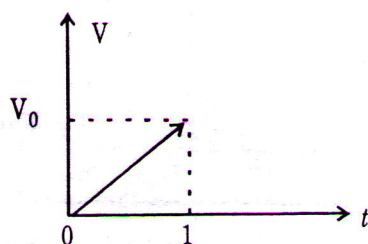


Fig. 1.

2. State and prove initial value theorem.
3. Obtain the input impedance $Z_{in}(s)$ for the circuit in Fig. 2. at (G) $s = 0$, (b) $s = j 4$ rad/sec.

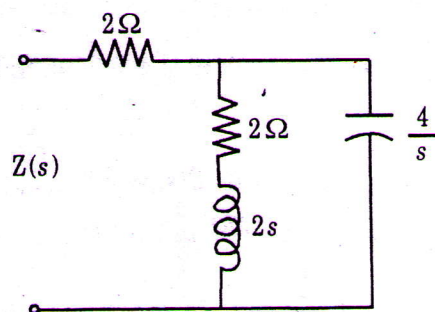


Fig. 2.

4. Construct the pole zero plot for the $H(s) = k \frac{s^2 + 50s + 400}{s^2 + 40s + 2000}$.

Turn over

5. Find the Z parameters of the two port circuit given in Fig. 3. :

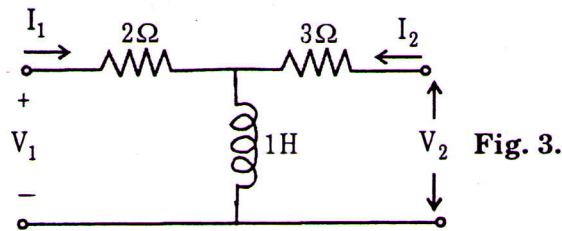


Fig. 3.

6. Find the transmission parameters of the Fig. 4 given, where Z_a and Z_b are non zero.

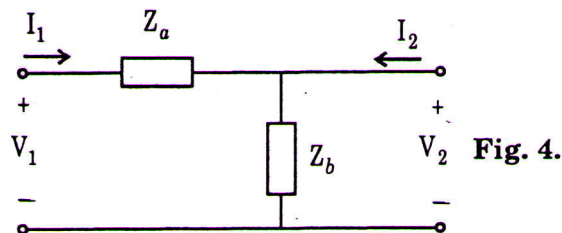


Fig. 4.

7. Derive the expression for : (a) characteristic impedance (b) the cut off frequency of a low pass filter.
8. What are the drawbacks of constant K prototype filters ? What is an m -derived section ?

(8 × 5 = 40 marks)

Part B

- II. (a) Find the inverse Laplace transform of each of the following functions :—

(i) $F(s) = \frac{2s + 4}{s^2 + 4s + 13}$

(ii) $F(s) = \frac{2s}{(s^2 + 4)(s + 5)}$

(6 marks)

- (b) Write the time domain equation and find $i_1(t)$ and $i_2(t)$ using Laplace transform methods in Fig. 5.

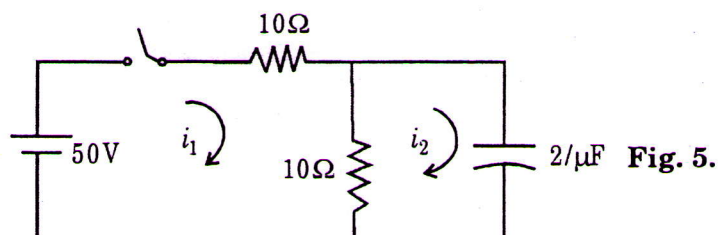


Fig. 5.

(9 marks)

Or



III. (a) A series RLC circuit with $R = 5\Omega$, $L = 0.2$ H, and $C = 1$ F has a voltage source $v = 10e^{-100t}$ applied at $t = 0$. Find the resulting current.


(b) Find the Laplace transform of :

(i) $e^{-at} \cos wt$;

(ii) $1 - e^{-at}$.

(5 marks)

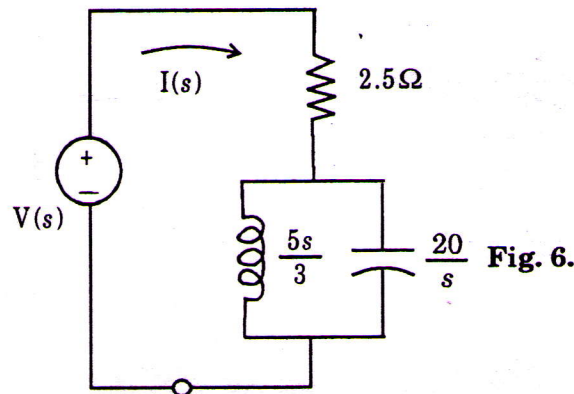IV. (a) A passive network in the s domain is given in Fig. 6. :



Obtain the network function for the current $I(s)$ due to an input voltage $V(s)$.


(10 marks)

(b) Express the impedance $Z(s)$ of the parallel combination of $L = 4$ H and $C = 1$ F at what frequencies 's' is this impedance zero or infinite ?

(5 marks)

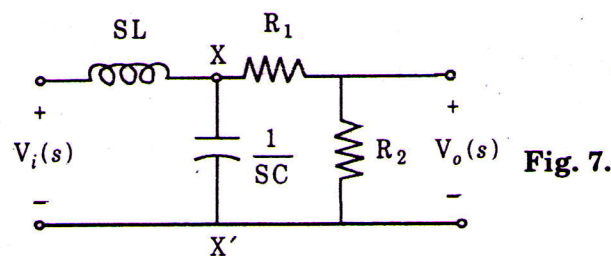V. For the two port network shown in Fig. 7. find the values of R_1 , R_2 and C given that the voltage

transfer function is $\frac{V_o(s)}{V_i(s)} = \frac{0.2}{s^2 + 3s + 2}$.



(15 marks)


Turn over

- VI. Give the defining equation of the hybrid parameters. Write the relations between the h parameters and ABCD parameters ? Why are the h parameters preferred in transistor equivalent circuit representation ?

(15 marks)

Or

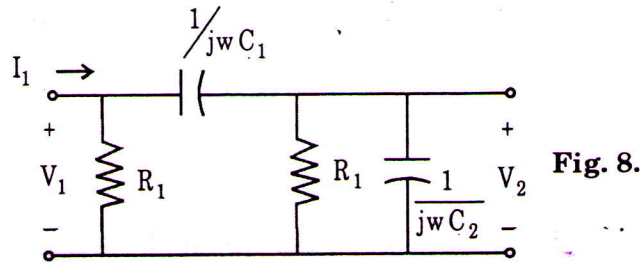- VII. Determine the y parameters of the circuit :



(15 marks)

- VIII. (a) Derive an expression for the cut off frequency of a T type high pass filter. (6 marks)
 (b) Calculate the values of the elements of a high pass filter having a cut off frequency of 1 kHz and operating into a load resistance of 600 Ω .

(9 marks)

Or

- IX. Design a prototype low pass filter of nominal characteristic impedance 600 Ω . Given that the poles of the transfer Impedance function of the filter terminated by the nominal characteristic impedance are $7.9 \times 10^3 (-1 \pm j 1)$. What is the cut off frequency of the filter ?

(15 marks)