

D 51494

(Pages : 2)

Name

Reg. No.

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE
EXAMINATION, DECEMBER 2008**

AI 04 306 – ELECTRONIC CIRCUITS

(2004 Admissions)

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

- I. (a) Among the three transistor configurations, which one do you think is best suitable for the following applications (i) impedance matching ; (ii) power amplifier. Give reasons to support your answer.
- (b) Draw the circuit diagram of emitter follower.
- (c) Derive the relationship between f_B and f_r .
- (d) Express your view about choice of transistor configuration in cascode amplifier.
- (e) Draw the structure and V.I. characteristics of UJT.
- (f) Differentiate between MESFET and MOSFET.
- (g) Define CMRR and input impedance of differential amplifier.
- (h) Draw the transfer characteristics of differential amplifier. Over what range does a differential amplifier acts as a good limiter?

(8 × 5 = 40 marks)

- II. (a) (i) What are the three different parameters of JFET? Explain briefly.
- (ii) Derive an expression for transconductance g_m of a JFET in terms of V_P , I_{DSS} and I_D .
- (iii) What is a Darlington pair? What is the practical limitation of Darlington circuit?

(6 + 5 + 4 = 15 marks)

Or

- (b) Obtain the expressions for current gain, voltage gain, power gain, input and output impedance of a CE amplifier.

(15 marks)

- III. (a) Draw the high frequency hybrid II model of a common Emitter transistor. What are the merits of the model? Discuss the validity of various components.

(15 marks)

Or

Turn over

- (b) Draw the circuit diagram of a cascode amplifier and explain the principle of operation. Derive an expression for output voltage V_0 .

(8 + 7 = 15 marks)

- IV. (a) Explain with neat diagram, the construction operation of a N-channel Enhancement MOSFET. (15 marks)

Or

- (b) Explain the construction, principle and V-I characteristics of UJT. Mention the advantages and applications.

(15 marks)

- V. (a) (i) Explain the significance of CMRR.
(ii) Write notes on GaAs amplifier.

(7 + 8 = 15 marks)

Or

- (b) Explain the working of BJT differential amplifier using small signal model.

(15 marks)

[4 × 15 = 60 marks]