

D 51545

Name.....

Reg. No.....



**FIFTH SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION
DECEMBER 2008**

EC/AI 2K 506 B/PTEC 2K 505 B—POWER ELECTRONICS

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

- I. (a) Define holding current is a thyristor.
(b) Explain the term "Forced Commutation" technique in a thyristor.
(c) What is the use of free wheeling diode in a converter circuit.
(d) Sketch the variation O/P voltage with respect to firing angle in 1 ϕ half controlled bridge rectifier.
(e) List out the applications of cycle converter.
(f) Define the Time ratio control in a chopper circuit.
(g) Define buck regulator.
(h) List out the applications of SMPS.
- (8 $\times$ 5 = 40 marks)
- II. (a) Draw and explain the two transistor analogy of a SLR. Also sketch the V I characteristics.
Or
(b) With a neat sketch explain the different triggering circuits of a SLR.
- III. (a) Describe the operation of a 1-phase fully controlled converter fed RL load.
Or
(b) With a neat sketch explain the 1-phase series and parallel inverter circuits.
- IV. (a) A single phase AC voltage regulator with RL load has the following details :
Supply voltage = 230 V, 50 Hz R = 4 Ω and WL = 3 Ω .
Calculate :
(i) Firing angle range.
(ii) Maximum value of RMS load current.
(iii) Maximum power and power factor.
(iv) The conduction angle for $\alpha = 0^\circ$ and $\alpha = 120^\circ$.
Or
(b) Explain in detail speed control schemes of DC motor.
- V. (a) Describe the operation of a buck regulator with a neat diagram.
Or
(b) Explain the operation of a online ups with suitable block diagram.

[4 $\times$ 15 = 60 marks]