

C 31679

(Pages : 2)

Name.....

Reg. No.....

**COMBINED FIRST AND SECOND SEMESTER B.TECH. (ENGINEERING)
DEGREE EXAMINATION, JUNE 2007**

IT/CS 2K 109—BASIC ELECTRICAL ENGINEERING

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

- I. (a) Give international system of units for energy, voltage, current, flux density and force.
- (b) State and explain Thevenin's Theorem.
- (c) Give restrictions on pole-zero locations for driving point functions.
- (d) Show that power consumed in a pure resistive circuit is not constant but it is fluctuating.
- (e) In a 25 kVA, 2000/200 V transformer the iron and full-load copper losses are 350 W and 400 W respectively. Calculate the efficiency at unity power factor at-(i) full-load and (ii) half-load.
- (f) Write short notes on : Wattmeters.
- (g) Derive the e.m.f. equation of a d.c. generator.
- (h) Explain the working principle of three-phase induction motors.

(8 × 5 = 40 marks)

- II. (a) Use Norton's theorem to find current and voltage across 50 Ω resistor in the network of Fig. 1.

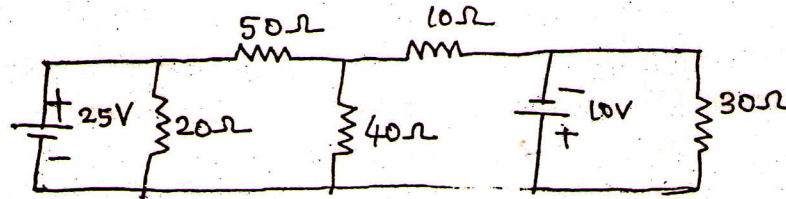


Fig. 1

Or

- (b) Use superposition theorem to find current through 3 Ω resistor in the network of Fig. 2.

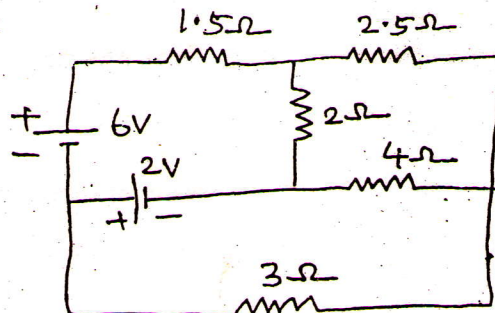


Fig. 2

Turn over

- III. (a) (i) A resistor R in series with a capacitor C is connected to a 240 V, 50 Hz supply. Find the value of C so that R absorbs 300 W at 100 V. Find also the maximum charge and maximum energy stored in C .

(8 marks)

- (ii) A coil resistance 10Ω and inductance 0.1 H is connected in series with a capacitor of capacitance $150 \mu\text{F}$ across a 230 V 50 Hz supply. Determine power factor, voltage across the coil and voltage across the capacitor.

(7 marks)

Or

- (b) In the network of Fig. 3, the switch is closed at $t = 0$. Find an expression for currents $i_1(t)$ and $i_2(t)$. Assume initial conditions are zero.

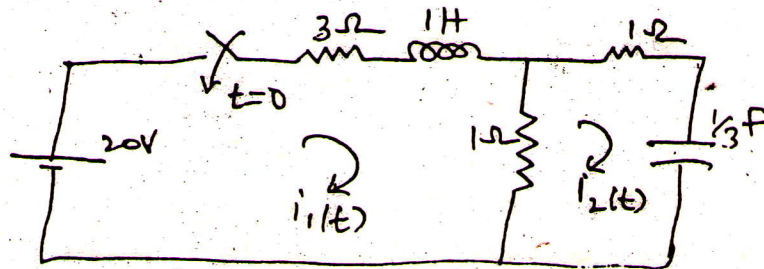


fig. 3

(15 marks)

- IV. (a) A 5 kVA, 200/400 V, 50 Hz single-phase transformer gave the following data :—

OC test (on LV side) : 200 V, 0.7A, 60 W.

SC test (on HV side) : 22 V, 16 A, 120 W

Obtain the equivalent circuit parameters of the transformer referred to LV and HV side. If the transformer operates on full-load, determine the percentage regulation at 0.8 p.f. leading.

Or

- (b) Draw a neat diagram and explain the working of a moving coil voltmeter. Show the scheme of connection if the meter range is to be extended.

(15 marks)

- V. (a) Name the various types of d.c. generators. Draw the circuit diagram and voltage equation for each case.

Or

- (b) Explain in detail the construction and working of three-phase alternators.

(15 marks)

[4 × 15 = 60 marks]