

C 31721

(Pages : 2)

Name.....


Reg. No.....

**COMBINED FIRST AND SECOND SEMESTER B.TECH. (ENGINEERING)
DEGREE EXAMINATION, JUNE 2007**

CS 04 109—BASIC ELECTRICAL ENGINEERING

(2004 admissions)

[Common for CS, IT, PT]

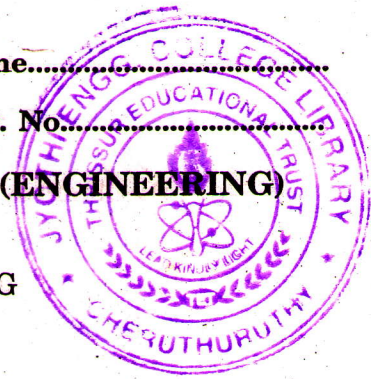


Time : Three Hours

Maximum : 100 Marks

Answer all questions.

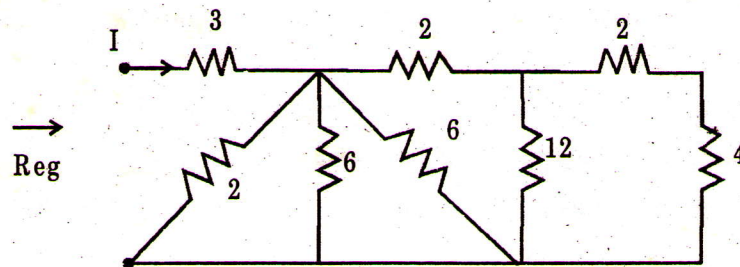I. (a) Determine Reg for the following circuit diagram :




All resistances are in ohms.

- (b) Obtain the equation for the current through any resistance, in a parallel circuit having n number of different resistances.
- (c) Compare the parameters of series and parallel resonances.
- (d) State and prove initial and final value theorems of Laplace transform.
- (e) Explain the different types of transformer.
- (f) Explain the following :—
 - (i) Cooling in autotransformer.
 - (ii) Voltage regulation of transformer.
- (g) Explain the construction of squirrel Cage induction motor.
- (h) Explain the principle of O-meter with a neat diagram.

(8 × 5 = 40 marks)

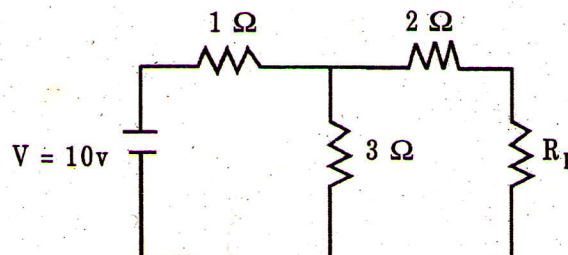- II. (a) (i) What are voltage and current sources ? Explain with examples. (7 marks)
- (ii) State and derive Thevenin's theorem. Apply Thevenin's theorem to the circuit diagram shown.



Or

(8 marks)

Turn over

- (b) (i) What are transients ? Explain. Obtain the response of RL transients. (7 marks)
(ii) Explain duality of networks with examples. (8 marks)
- III. (a) (i) Obtain average value and peak value, peak factor and form factor for a full wave rectified voltage wave. (7 marks)
(ii) Explain star-delta connections with an example. (8 marks)

Or

- (b) Explain the procedure of measuring 3 ϕ power using two wattmeter method with a neat diagram. (15 marks)
- IV. (a) (i) Derive the e.m.f. equation of a transformer. (7 marks)
(ii) Compare the parameters of electric circuits with magnetic circuits. (8 marks)

Or

- (b) (i) Derive an expression for Back e.m.f. of DC motor. (7 marks)
(ii) Explain the characteristics of DC motor and DC generator. (8 marks)
- V. (a) Describe in detail the types and constructional features of synchronous machines with neat sketches.

Or

- (b) Write technical notes on :
- (i) Induction type energy meter. (7 marks)
(ii) Moving-coil voltmeter and Ammeter. (8 marks)

[4 \times 15 = 60 marks]