

C 31824

(Pages : 3)

Name.....

Reg. No.....

**FOURTH SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION**  
**JUNE 2007**

**EE 04 403—ELECTRICAL MEASUREMENTS AND MEASURING INSTRUMENTS**

(2004 admissions)

Time : Three Hours

Maximum : 100 Marks

*Assume suitable data required, if any.*

*Answer all the questions.*

- I. (a) What are the various techniques by which damping torque is produced in an indicating instrument? Briefly explain those techniques.
- (b) Give the advantages and disadvantages of Instrument Transformers as compared to shunts and Multipliers used for the extension of instrument Range.
- (c) Derive the expression for the capacitance to be connected across the resistor in the pressure coil circuit of a dynamometer type Wattmeter so as to neutralize the effect of inductance of Pressure coil circuit.
- (d) Explain the sources of errors in Single-Phase induction type Energy Meters.
- (e) In a test for a fault to earth by Murray loop test, the faulty cable has a length of 5.2 km. The faulty cable is looped with a sound cable of the same length and cross-section. The resistances of ratio arms are  $100 \Omega$  and  $41.2 \Omega$  at balance. Calculate the distance of the fault from the test end. If the decade resistance boxes forming the ratio arms have limits of error of  $\pm 0.5 \%$  (standard deviation) of the dial reading, what is the limit of error in the above calculated result?
- (f) In a Carey-Foster's bridge a resistance of  $1.0125 \Omega$  is compared with a standard resistance of  $1.0000 \Omega$ , the slide wire has a resistance of  $0.250 \Omega$  in 100 divisions. The ratio arms nominally each  $10 \Omega$ , are actually  $10.05 \Omega$  and  $9.95 \Omega$  respectively. How far (in scale divisions) are the balance positions from those which would obtain if ratio arms were true to their Nominal value? The slide wire is 100 cm. long.
- (g) Explain the term "Standardization" of a potentiometer. Describe the procedure of standardization of a d.c. potentiometer.
- (h) An iron ring of  $350 \text{ mm}^2$  cross-sectional area with a mean length of 1 m. is wound with a magnetising winding of 100 turns. A secondary coil with 200 turns of wire is connected to a ballistic galvanometer having a constant of  $1 \mu\text{C}$  per scale division, the total resistance of the secondary circuit being  $2000 \Omega$ . On reversing a current of 10 A in the magnetising winding, the galvanometer shows a deflection of 100 scale divisions. Calculate the flux density in the specimen, and the value of permeability at this flux density.

(8 × 5 = 40 marks)

- II. (a) Explain the construction and Working of Permanent Magnet Moving Coil Meter with the help of neat sketch. Derive its torque equation.

(15 marks)

Or

Turn over

- (b) (i) A moving coil ammeter has a fixed shunt of  $0.02 \Omega$  with a coil resistance of  $R = 1000 \Omega$  and a potential difference of  $500 \text{ mV}$  across it and full scale deflection is obtained
- To what shunted current does this correspond ?
  - Calculate the value of  $R$  to give full scale deflection when shunted current  $I$  is
    - $10 \text{ A}$  ;
    - $75 \text{ A}$  ;
    - and (c) with what value of  $R$  is 40% deflection obtained with  $I = 100 \text{ A}$  ?

(10 marks)

- (ii) A permanent magnet Moving Coil Ammeter is connected across appropriate points of a bridge having Resistance of each arm of  $35 \Omega$  and connected across a supply of voltage,  $V = 5 \sin \theta + 0.2 \sin 3\theta$ . Determine the reading of the Ammeter if its resistance is  $30 \Omega$ .

(5 marks)

- III. (a) Explain the construction and working of Electro-resonance type frequency meters. Also draw the phasor diagrams.

(15 marks)

Or

- (b) (i) Explain how the Overload compensation is made in a single-phase induction type energy meter.

(5 marks)

- (ii) A dynamometer type wattmeter is used for measurement of power in a single-phase circuit: The load voltage is  $100 \text{ V}$  and the load current is  $9 \text{ A}$  at a lagging power factor of  $0.1$ . The wattmeter voltage circuit has a resistance of  $3000 \Omega$  and an inductance of  $30 \text{ mH}$ . Estimate the percentage error in the wattmeter reading when the pressure coil is connected : (a) on the supply side ; and (b) on the load side. The current coil has a resistance of  $0.1 \Omega$  and negligible inductance. The frequency is  $50 \text{ Hz}$ . Comment upon the result.

(10 marks)

- IV. (a) (i) Describe the Murray loop test for localization of ground and short circuit faults in cables.

(5 marks)

- (ii) Derive the equations for balance in the case of Maxwell's inductance capacitance bridge. Draw the phasor diagram for balance conditions.

(10 marks)

Or

- (b) A modified form of Wheatstone bridge is shown in Fig. 1. Calculate the value of unknown resistance,  $R_x$ , if  $R_a = 1200 \Omega$ ,  $R_b = 1600 \Omega$ ,  $R_1 = 800 \Omega$ ,  $R_2 = 1.25 R_3$  and  $R_3 = 0.5 R_b$  are the resistance values under balanced conditions :


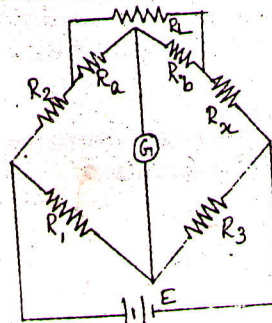


Fig. 1

(15 marks)

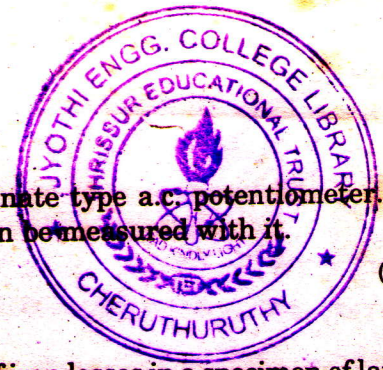

- V. (a) Describe the construction and working of a co-ordinate type a.c. potentiometer. How is it standardized? Explain how an unknown voltage can be measured with it.

(15 marks)

Or

- (b) Describe the Lloyd Fisher square for measurement of iron losses in a specimen of laminations. Describe how corrections for resistance of wattmeter pressure coil resistance and resistance of secondary winding are applied.

(15 marks)

[4 × 15 = 60 marks]