

EE  
D 41981

Name.....

Reg. No.....

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE  
EXAMINATION, DECEMBER 2007**

EE 2K 306—ELECTRICAL MEASUREMENTS AND MEASURING AND INSTRUMENTS

Time : Three Hours

Maximum : 100 Marks

*Answer all eight questions of Module I.  
Answer one questions each of module II-V.*

- I. 1 What are the various control arrangements made in indicating instruments ?  
2 Draw the diagram of a true rms voltmeter circuit and explain.  
3 Write about the error and compensation done in wattmeters.  
4 What is a trivector meter ? Where is it used ?  
5 Draw carry Foster slide wire bridge and write its merits.  
6 What is meant by earth resistance ? How is it measured ?  
7 Sketch the modern form of a potentiometer and say its merits.  
8 What is core loss ? How is this measured ?

(8 × 5 = 40 marks)

- II. 1 Draw a rectifier type meter and explain the factors influencing its performance.

*Or*

- 2 What are instrument transformers ? Where are they used ? How are they different from current transformers ?

- III. 1 Explain the principle and working of 3 phase energy meter.

*Or*

- 2 Explain with diagrams : (i) frequency meter. (ii) p.f. meter.

- IV. 1 Define sensitivity of dc bridges. What is the effect of interchanging battery and galvanometer of a bridge ? Explain.

*Or*

- 2 How is localization of cable fault done using the Murray and Varley loop tests ? Explain with necessary diagrams.

- V. 1 What are the principles of potentiometers ? Explain in detail.

*Or*

- 2 What is a Hall effect gaussmeter ? Explain its application.

(4 × 15 = 60 marks)