

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE
EXAMINATION, DECEMBER 2007**

EC/AI 04 303—ELECTRIC CIRCUIT AND NETWORK THEORY


(2004 admissions)

Time : Three Hours


Part A

Answer all the questions.

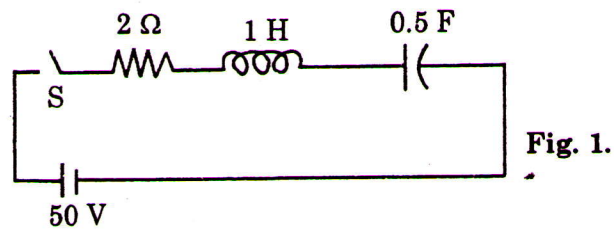
- I. 1 In the circuit given there is no initial charge on the capacitor if the switch is closed at $t = 0$, determine the resulting current.



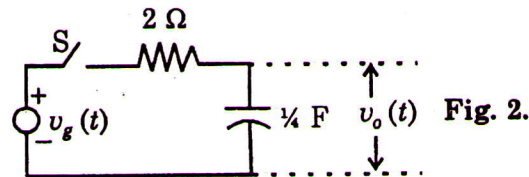- 2 For the initially inert network, the excitation is $v_g(t) = \frac{1}{2} \cos t u(t)$. Determine the free and forced response parts of $v_o(t)$.




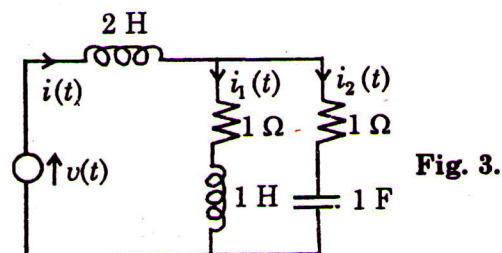- 3 Determine the driving point impedance function of the given circuit.




Turn over

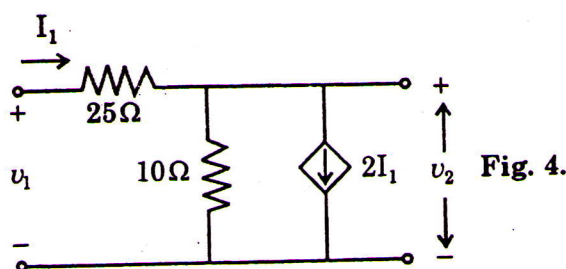- 4 Plot the following poles on S-plane and determine the nature of time response of the individual poles. Assume response to be current. $S_1 = 1 \pm j1$, $S_2 = 2 \pm j2$.
- 5 Find the four 'y' parameters for the given network.



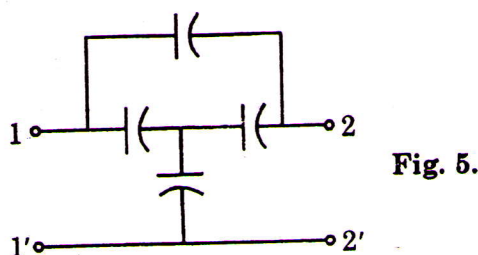- 6 Apply the T - π transformation to obtain an equivalent T network for the capacitive network given in the figure.



- 7 It is required to find a transfer function for a low-pass filter to satisfy the following specifications :
- The end of the pass band is 10 kHz.
 - The peak to peak ripple in the pass band must not exceed 1dB.
 - At 60 kHz the response must be down atleast 50 dB from its peak value in the pass band.
- 8 Design a π type attenuation to give an attenuation of 50 dB and to work in a line of 600Ω impedance.

(8 \times 5 = 40 marks)

Part B

- II. (a) State and prove initial and final value theorem. (6 marks)
- (b) A periodic function with $T = 5$ has the values : $f(t) = 0$, $0 < t < 1$, and $3 < t < 5$ and $f(t) = 3 + \delta(t - 3)$, $1 < t < 3^+$ find its Laplace transform. (5 marks)
- (c) Determine $f(t)$ if :

(i) $F(s) = \frac{s}{s^2 + 4}$,


(ii) $\frac{8s - 2}{s^2 - 6s + 10}$.

(4 marks)

Or



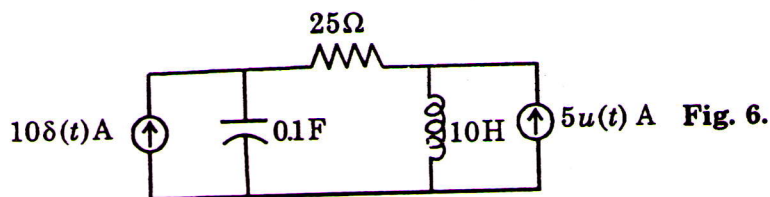III. (a) Find $i(t)$ in the given circuit.



(7 marks)


(b) Find both the initial and final values of the time functions :

(i) $\frac{8s - 2}{s^2 + 6s + 10}$

(ii) $\frac{2s^3 - s^2 - 3s - 5}{s^3 + 6s^2 + 10s}$

(8 marks)

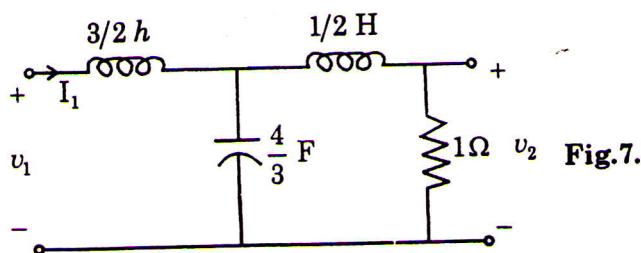
IV. Determine the transfer impedance, driving point impedance and voltage transfer function of the given network.



(15 marks)

Or

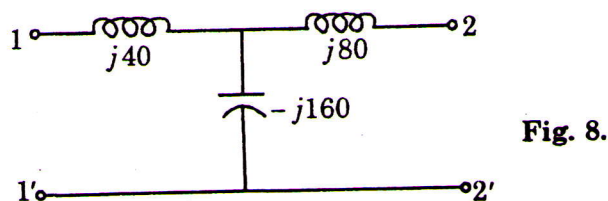V. Find ABCD constants and show that $AD - BC = 1$, for the given network.



(15 marks)

VI. Discuss in detail about the different methods of interconnection of two port networks. (15 marks)

Or

VII. Derive expressions for the elements of a T network in terms of known z parameters of a two port network.

(15 marks)

Turn over

VIII. Synthesize (a) a band-pass filter ; (b) a band stop filter with maximally flat ($n = 4$) amplitude response with $\omega_{c_2} = 8 \times 10^4$ Hz and $\omega_{c_1} = 2 \times 10^4$ Hz.

(15 marks)

Or

IX. Discuss in detail about the different types of filters.

(15 marks)

[4 × 15 = 60 marks]