

D 26591

Name.....

Reg. No.....

**COMBINED FIRST AND SECOND SEMESTER B.TECH.
(ENGINEERING) DEGREE EXAMINATION, DECEMBER 2006**

EC 04-108—BASIC ELECTRONICS

((EC, BM, BT, AI, IC)

[2004 admissions]



Time : Three Hours

Maximum : 100 Marks

Answer all questions.

Each correct answer carries 5 marks.

- I. 1 What is electron ballistics ?
2 How does multimeter measure voltage ? Explain.
3 What are the characteristics of inductor ?
4 Bring out the differences in the reverse bias characteristics of ordinary junction diode and zener diode. Why do the differences exist ?
5 What is the effect of 2 point location on allowable signal swing ?
6 How is 2 point chosen ? Explain.
7 Why is transformer utility factor of half wave rectifier and center tapped full wave rectifier lesser than bridge type rectifier ?
8 What is the drawback of C filter ? How is it rectified ?

Answer all questions.

Each correct answer carries 15 marks.

- II. 1 Explain the principle of operation of a pentode.

Or
2 What are the two focussing used in CRTs ? Explain.
III. 1 What are the different types of capacitors ? Explain their characteristics.

Or

- 2 Draw the two types of biased-clippers and explain their operation.
IV. 1 Analyse the operation of BJT graphically.

Or
2 What are the different compensation circuits used in BJT amplifiers ? Explain any two.
V. 1 Define and compare the following for a HWR and center tapped FWR :
Ripple factor, PIV, efficiency and rectification factor.

Or

- 2 What is a π -filter ? Emphasize its importance.