

D 26595

(Pages : 2)

Name


Reg. No.

**COMBINED FIRST AND SECOND SEMESTER B.TECH. (ENGINEERING)
DEGREE EXAMINATION, DECEMBER 2006**

EE 04-109—BASIC ELECTRICAL ENGINEERING

(2004 admissions)

[AI/EE/EC/IC/BM/BT]

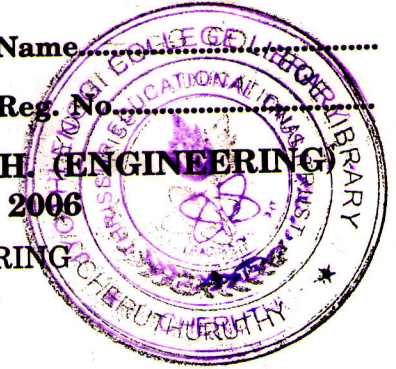

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

Part A


1. (a) What are dependent and independent sources ? Explain with examples.
(b) State and explain superposition theorem.
(c) Explain the concept of electromagnetic force with the help of relevant rules.
(d) What is leakage coefficient ? How does it affect magnetic circuits ? What are its disadvantages ?
(e) Explain the generation of sinusoidal e.m.f. with a neat sketch. Obtain the mathematical representation of it.
(f) Define (i) Bandwidth ; (ii) Q factor ; (iii) Resonant frequency. Obtain the relation among them.
(g) What are 3 wire and 4 wire systems ? Explain with examples.
(h) Explain the principle of measurement of 3ϕ power using 2 wattmeter method.

(8 × 5 = 40 marks)

2. (a) (i) 3 resistors 4Ω , 12Ω and 6Ω are connected in parallel. If the total current taken is 12 A, find the current through each resistor. (8 marks)
(ii) What are the advantages of series, parallel and series parallel circuit ? Explain the characteristics of a series and parallel circuit. (7 marks)

Or

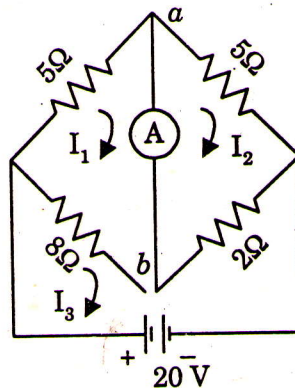- (b) (i) State and explain Norton's theorem. (8 marks)
(ii) In the circuit shown in figure, compute the current through the "O" resistance ammeter. Use Norton's theorem.



(7 marks)

Turn over

