

D 26618

(Pages : 3)

Name

Reg. No.

COMBINED FIRST AND SECOND SEMESTER B.TECH. (ENGINEERING)
DEGREE EXAMINATION, DECEMBER 2006

IT/CS 2K 109—BASIC ELECTRICAL ENGINEERING

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

- I. (a) Find the resistance of a coil of mean diameter 3 cm. containing 200 turns of manganin wire 0.05 cm. in diameter. The resistivity of manganin is $42 \mu\Omega - \text{cm}$.
(b) State and explain superposition's, theorem.
(c) A two branch parallel circuit has a resistance and inductance in one branch and a capacitance in the other. The transfer impedance of the circuit is $Z(s) = \frac{10^6 (s + 10)}{s^2 + 10s + 5 \times 10^6}$

Find parameters of the circuit.

- (d) Describe what do you understand by real power, reactive power and apparent power.
(e) Describe various losses in a transformer and also define efficiency.
(f) Explain the principle of working of a moving iron instrument.
(g) Explain the principle of action of a d.c. generator.
(h) In a given d.c. machine, if $p = 4$; $Z = 400$, $N = 300$ r.p.m. and $\phi = 100 \text{ mwb}$ calculate E_g with winding (i) lap-connected and ; (ii) wave-connected.

(8 × 5 = 40 marks)

- II. (a) Use Norton's theorem to find current and voltage across 44Ω resistor in the Network of Fig. 1 (given below) :

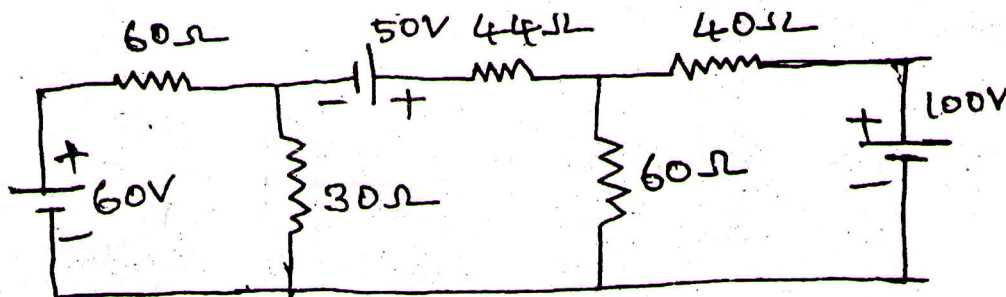


Fig.1

(15 marks)

Or

Turn over

- (b) Use superposition theorem to find current through $4\ \Omega$ resistor in the network of Fig. 2 (given below) :

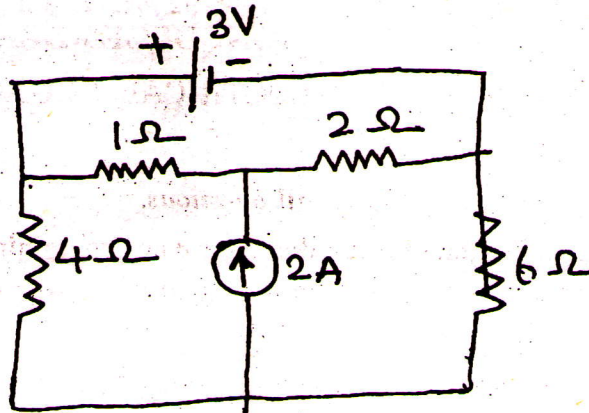


Fig. 2

(15 marks)

- III. (a) (i) A coil of power factor 0.6 is in series with a $80\ \mu\text{F}$ capacitor. When connected to a 60 Hz supply, the voltage across the capacitor is equal to the voltage across the coil. Find the resistance and reactance of the coil.

(7 marks)

- (ii) Two impedances given by $Z_1 = (5 + j5)\ \Omega$ and $Z_2 = (5 - j5)$ are connected in parallel across a voltage $200\angle 0^\circ\ \text{V}$. Calculate the branch currents and the total current. Also calculate the total power consumed.

(8 marks)

Or

- (b) In the circuit of Fig. 3, (given below) find $i_1(t)$ and $i_2(t)$ when the switch is closed. Assume initial current is zero.


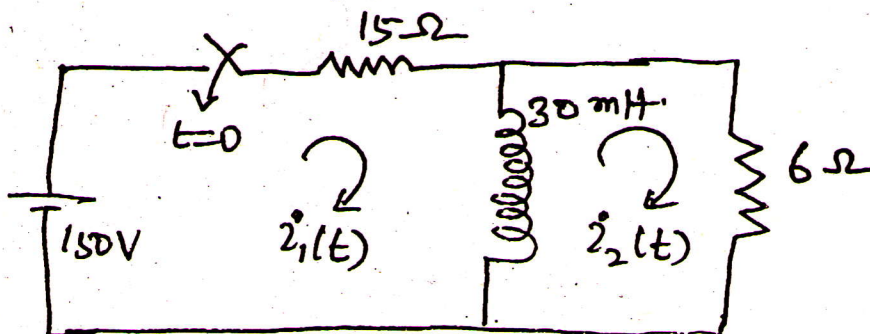


Fig. 3

(15 marks)

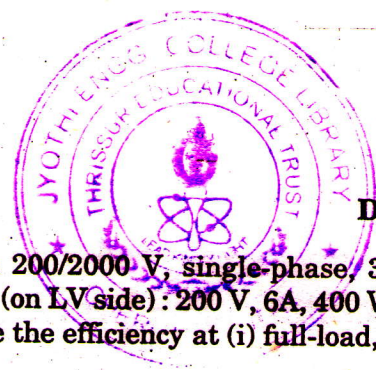

- IV. (a) Obtain the approximate equivalent circuit of a given 200/2000 V, single-phase, 35 kVA transformer having the following test results : OC Test : (on LV side) : 200 V, 6 A, 400 W. S.C. Test : (on H V side) = 75 V, 18 A, 650 W. Also calculate the efficiency at (i) full-load, 0.8 pf. and (ii) half-load, UPF.

(15 marks)

Or

- (b) Describe with neat sketch and working principle of a dynamometer type wattmeter and show its connections.

(15 marks)

- V. (a) Explain the principle of working of a synchronous motor. Also explain how a synchronous motor is made self-starting.

(15 marks)

Or

- (b) Show that a rotatory mmf. is produced in the stator of a 3-phase induction motor when 3-phase voltage is applied to its stator winding. Also explain the principle of working of three-phase induction motor.

(15 marks)

[4 × 15 = 60 marks]