

C 5775

(Pages : 4)


Name.....

Reg. No.....

COMBINED FIRST AND SECOND SEMESTER B.TECH. (ENGINEERING)  
DEGREE EXAMINATION, JUNE 2005

AI2K 109. BASIC ELECTRICAL ENGINEERING

(Common to EE, EC, IC, BM and BT)

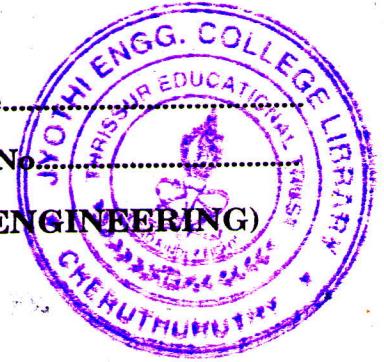

Time : Three Hours

Maximum : 100 Marks

1. (a) State and explain Kirchoff's voltage law with an example.
- (b) Differentiate between electric and magnetic circuits.
- (c) State and prove superposition theorem.
- (d) A series R-L circuit with  $R = 30 \Omega$  and  $L = 15 H$  has a constant voltage of  $V = 60 V$  applied at  $t = 0$  as shown in Fig. 1. Determine the current, the voltage across resistor and inductor.

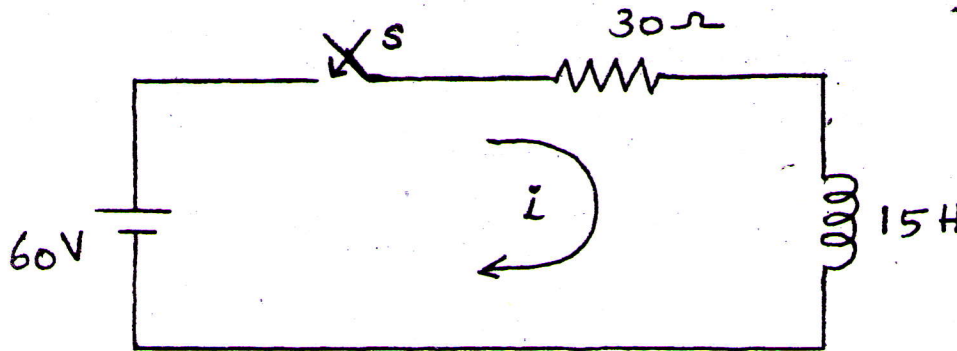


Fig. 1

- (e) Discuss how half power frequencies can be related to bandwidth.
- (f) Define active power and reactive power with expressions.
- (g) Differentiate between single-phase and three-phase system.
- (h) Each phase of 3- $\phi$  alternator produces a voltage of 6351 volts and carry a max. current of 315 A. Find the line voltage, maximum line current and total kVA capacity of the alternator if it is (i) star connected and (ii) delta connected.

(8  $\times$  5 = 40 marks)

Unit I

2. (a) (i) When a d.c. voltage is applied to a capacitor, the voltage across its terminals is found to build up in accordance with  $v_c = 50(1 - e^{-100t})$ . After the lapse of 0.01 s, the current flow is equal to 2 mA. What is the value of capacitance in microfarads and how much energy is stored in the electric field at this time ?

(6 marks)

Turn over

(ii) What is the voltage across A and B in the circuit shown in Fig. 2 ?

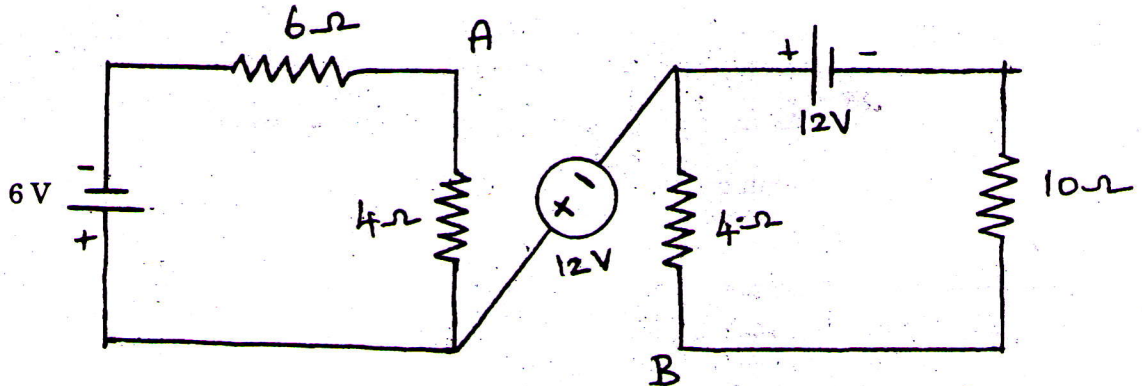


Fig. 2

(9 marks)

Or

(b) Determine the current delivered by the source in the circuit shown in Fig. 3.

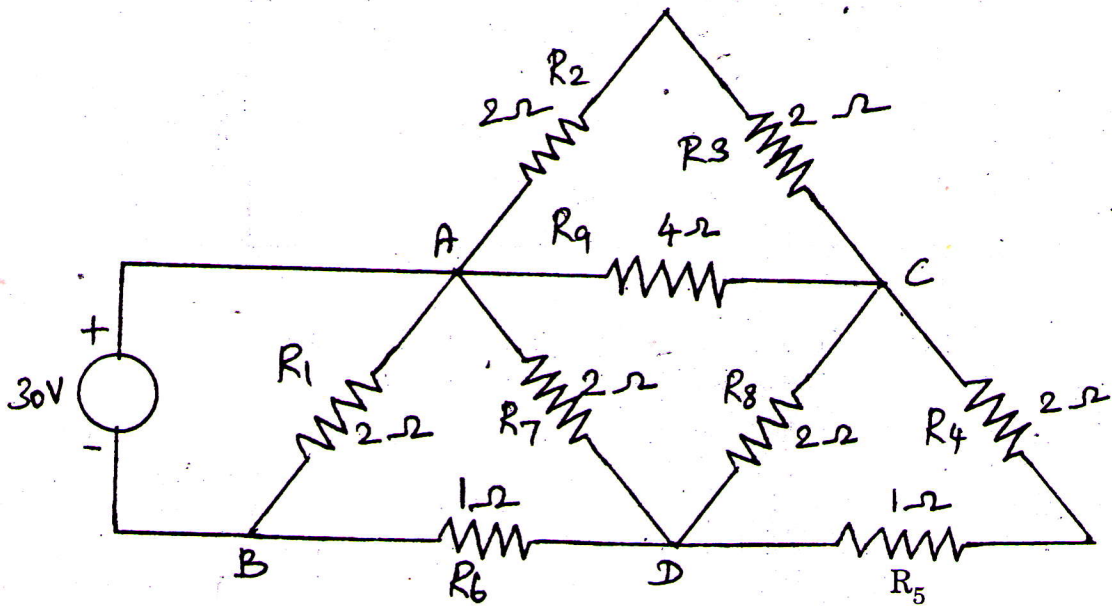


Fig. 3

(15 marks)

Unit II

3. (a) (i) A  $5\ \Omega$  resistance and  $20\ \text{H}$  inductance are connected in series across a battery. At the instant of closing the switch, the current increases at the rate of  $4\ \text{A/s}$ . Find the supply voltage, rate of growth of current when  $5\ \text{A}$  flows in the circuit and the energy stored under both conditions.

(6 marks)