

C 5776

(Pages 4)

Name.....

Reg. No.....



**COMBINED FIRST AND SECOND SEMESTER B.TECH. (ENGINEERING)
DEGREE EXAMINATION JUNE 2005**

CS 2K 109/IT 2K 109—BASIC ELECTRICAL ENGINEERING

Time : Three Hours

Maximum : 100 Marks

Part A

I. (a) What is the voltage across A and B in the circuit shown in Fig (1).

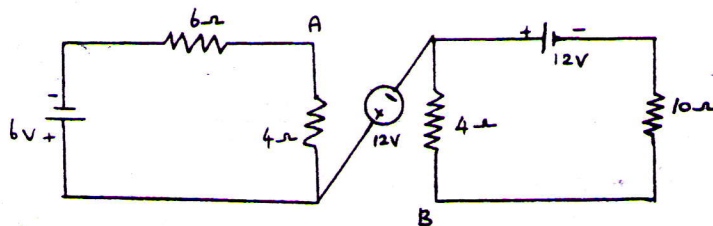


Fig. 1

(b) Obtain the Thevenin's equivalent circuit for the network shown in Fig. (2).

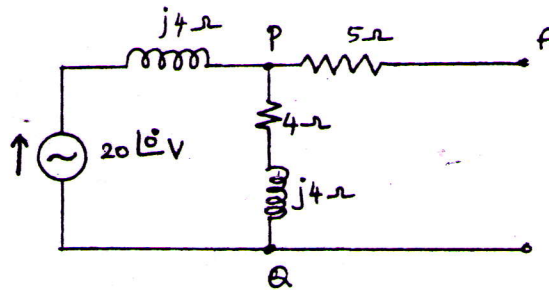


Fig. 2

(c) A series RC circuit consists of resistor of 10Ω and capacitor of 0.1 F as shown in Fig. (3). A constant voltage of 20 V is applied to the circuit at $t = 0$. Obtain the current equation. Determine the voltage across the resistor, and the voltage across the capacitor.

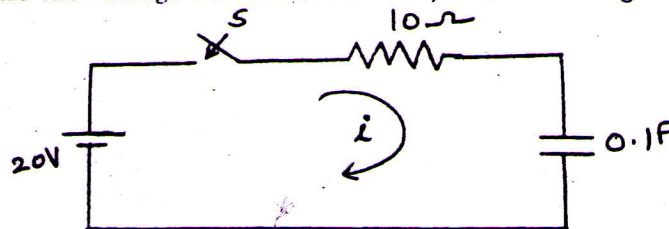


Fig. 3

Turn over

- (d) Explain natural and forced response.
 (e) Make a comparison between electric and magnetic circuits.
 (f) Explain the concept of mutual inductance behind the principle of transformer.
 (g) Differentiate between Slip-ring and Cage IM.
 (h) Write about the different types of d.c. generators.

(8 × 5 = 40 marks)

Part B**UNIT I**

- II. (a) Determine the voltage V_{AB} in the circuit shown in Fig. (4).

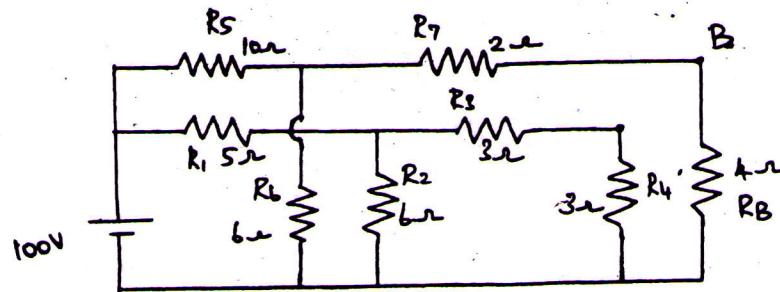


Fig. 4

(15 marks)

Or

- (b) Find the voltage across the $2\ \Omega$ resistor by using superposition theorem as shown in Fig. (5).

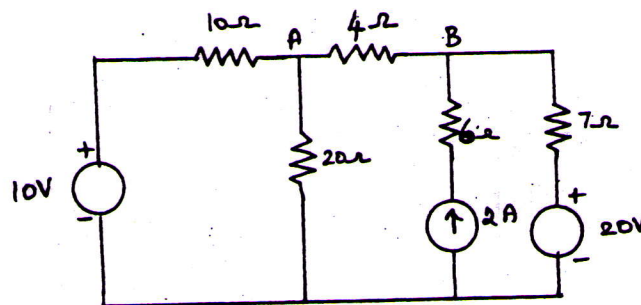


Fig. 5

(15 marks)

UNIT II

- III. (a) The circuit shown in Fig. (6) consists of R-L series elements with $R = 150 \Omega$ and $L = 0.5 \text{ H}$. The switch is closed when $\phi = 30^\circ$. Determine the resultant current when voltage $V = 50 \cos(100t + \phi)$ is applied to the circuit at $\phi = 30^\circ$.

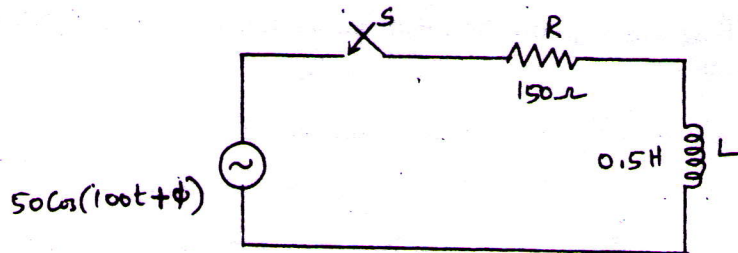


Fig. 6

Or

- (b) For the network shown in Fig. (7) determine the transfer functions $G_{21}(s)$ and $Z_{21}(s)$. Also find the driving point impedance, $Z_{11}(s)$.

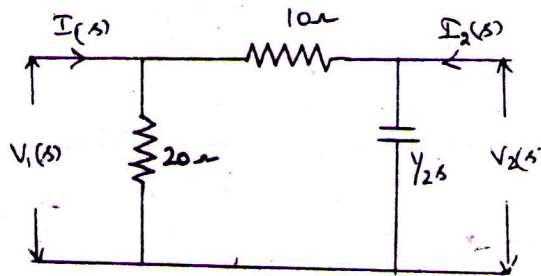


Fig. 7

(15 marks)

UNIT III

- IV. (a) (i) Derive from the first principles the e.m.f. equation of a transformer.
 (ii) Explain with suitable expression the condition for maximum efficiency.

(15 marks)

Or

- (b) Discuss in detail the construction and working of Electrodynamometer type wattmeter with a neat sketch and with relevant expressions (if any).

(15 marks)

Turn over

UNIT IV

- V. (a) Explain the construction and principle of operation of an alternator with relevant diagrams mentioning its applications.

(15 marks)

Or

- (b) With a neat diagram, explain the construction and working of a d.c. motor. Also enumerate its applications.

(15 marks)

[4 × 15 = 60 marks]