

D 1816

(3 pages)

Name.....

Reg. No.....

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINATION
DECEMBER 2004**

EC-2K-302 – ELECTRIC CIRCUITS AND NETWORK THEORY

(New Scheme)

Time : Three Hours

Maximum : 100 Marks

Answer all eight questions in I.

- I. (a) Find the Norton's equivalent for the circuit shown in Fig.1 at terminals AB.

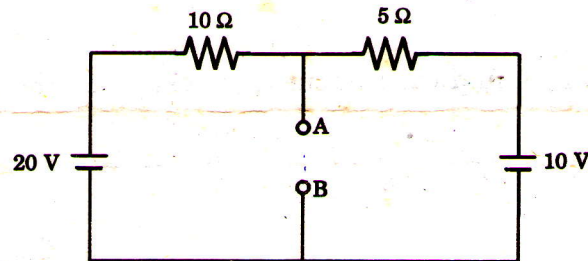


Fig. 1

- (b) Find the impulse response of a simple RC network.
- (c) What is convolution integral ? Explain.
- (d) What are the necessary conditions to be satisfied by the transfer function ?
- (e) What are the characteristics of symmetrical network ?
- (f) Draw the n -parameter equivalent circuit for a two-port network. Explain its parameters.
- (g) What are the properties of positive real function ?
- (h) What are the applications of maximum module theorem ?

(8 × 5 = 40 marks)

Turn over

Answer either (a) or (b) of questions II to V.

- II. (a) Determine voltage V which causes the current I_1 to be zero in the following Fig.2.

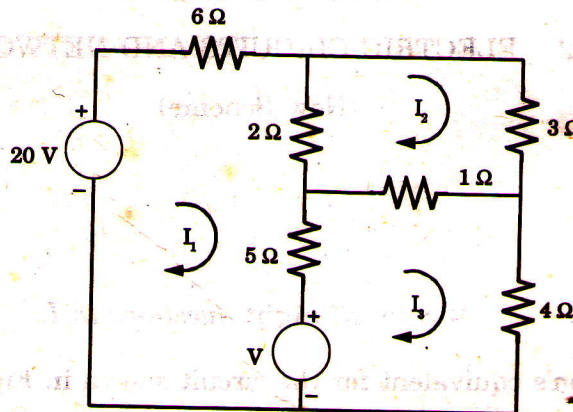


Fig. 2

Or

- (b) In the following Fig.3, find the current transient when the switch is closed at $t = 0$.

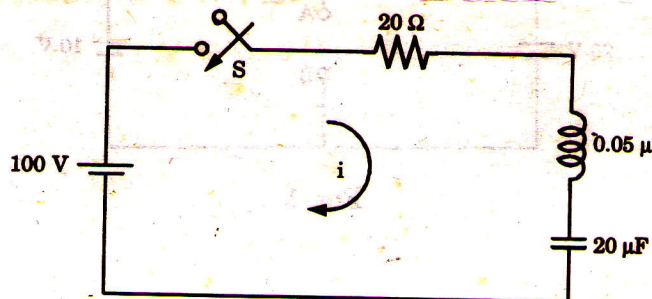


Fig. 3

(15 marks)

- III. (a) Explain how R, L and C can be transformed as admittance in S-domain. (6 marks)
- (b) Using Mesh analysis find the value of V_2 in the following Fig.4 such that current in the impedance $(3 + j4 \Omega)$ is zero.

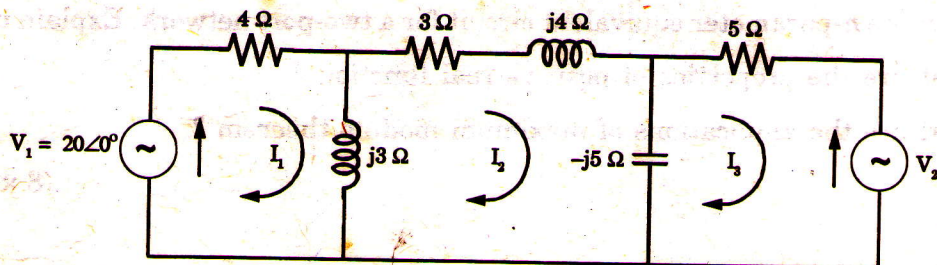


Fig. 4

(9 marks)

Or



- (b) Draw the pole zero diagram for the given network function $I(s)$ and hence obtain $i(t)$

$$I(s) = \frac{20s}{(s+5)(s+2)}$$

(9 marks)

Determine the transfer functions $Z_{21}(s)$ and $G_{21}(s)$ for the network in Fig. 5.

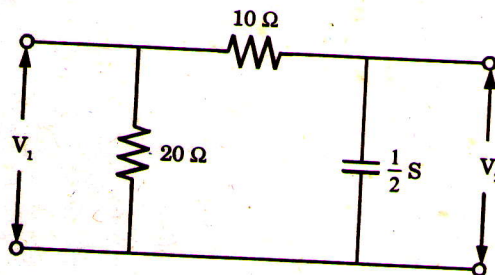


Fig. 5

- IV. (a) Find the characteristic impedance and propagation constant of symmetrical T and π networks. What is the relation between Z_0 of T and π networks? (6 marks)

Or

- (b) Design a composite row pass filter for the following specifications with suitable terminating half section.

$$f_c = 4 \text{ kHz} \quad f_{\infty} = 5 \text{ kHz} \quad R = 500 \Omega.$$

- V. (a) Explain about Strun's theorem. (15 marks)

Determine whether the following polynomial is a Hurwitz polynomial

$$P(s) = 2s^6 + s^5 + 13s^4 + 6s^3 + 56s^2 + 25s + 25.$$

Or

- (b) Design the first and second Foster form LC network for the following transfer function.

$$Z(s) = \frac{(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

(15 marks)

(4 × 15 = 60 marks)