D 1818

(2 pages)

Reg. No....

Name

## THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE EXAMINA DECEMBER 2004

## EC-2K/PT-2K-304 - BASIC ELECTRONICS

(New Scheme)

Time : Three Hours

Ι,

II.

Maximum : 100 Marks

- (a) State and Explain Child-Langmuir law.
  - (b) Explain the principles of secondary Emission.
- (c) Draw a CRC filter circuit write its ripple factor expression. Explain the filter action.
- (d) Define and explain :
  - (i) Ripple factor, (ii) Rectification efficiency, (iii) PIV.
- (e) What are dc restorers ? Write their types. Mention the pótential applications of dc restorers.
- (f) Draw the block diagram of a controlled transistor regulator. Explain its advantages.
- (g) Draw the hybrid  $\pi$  model of CE configuration BJT. Define the parameters of the circuit.
- (h) Explain the advantages of hybrid parameters applied to transistors.

 $(8 \times 5 = 40 \text{ marks})$ 

- (a) (i) Explain the construction of pn junction diodes. (8 marks)
   (ii) Explain in detail the V-I characteristics of diodes. State the potential applications
  - of pn junction diodes. (7 marks)
- (b) Derive Richardson's equation. (15 marks)
  III. (a) Write short notes on :

Or

(i) Types of transformers.(8 marks)(ii) M-phase rectifiers.(7 marks)

Or

- (b) Draw a neat circuit diagram of a bridge rectifier and explain its principle of operation with neat waveforms. Derive expressions for ripple factor and rectification efficiency. (15 marks)
- IV. (a) (i) Show and explain Zener diode as a voltage regulator. (8 marks)
  - (ii) Draw a neat circuit diagram of voltage tripler. Explain its principle of operation. (7 marks)

Turn over

D 1818

## Or

2

(b) Explain the following diode circuits.

(i) Clamper. (ii) Limiter. (8 + 7 = 15 marks)

Or

(a) Draw the n-parameter equivalent circuit of common base configuration transistor. Derive expressions for voltage gain, current gain, Input and Output Impedances.

144 第二日 18 million

(15 marks)

(b) Write technical notes on :

.

F

V.

2

?

(i) Effect of temperature on MOSFET model parameters.

(ii) Equivalent circuit of CD configuration MOSFET.

(8 marks) (7 marks)