

E.C

D 1940



FIFTH SEMESTER B. Tech. (ENGINEERING) DECEMBER
EXAMINATION, DECEMBER 2004

EC 2K-504—LINEAR INTEGRATED CIRCUITS

Time : Three Hours

Maximum : 100 Marks

*Answer all questions.
Each correct answer carries 5 marks.*

- I.
- 1 Define PSRR and mention its ideal and practical values.
 - 2 Define virtual ground and explain its use.
 - 3 What is the advantage of current source as load ?
 - 4 What is meant by wide swing ?
 - 5 Draw non-inverting amplifier using opamp and derive the expression for its input resistance.
 - 6 What is zero crossing comparator ? Mention one of its uses.
 - 7 What is Butterworth filter ? Why is this preferred mostly ?
 - 8 What is Antoniou's gyrator ?

(8 × 5 = 40 marks)

*Answer all questions.
Each correct answer carries 15 marks.*

- II.
- 1 Draw a differential amplifier circuit utilizing a Darlington pair and explain its operation. What are its merits ?
- Or
- 2 How is slew rate and CMRR measured in laboratory ? Explain with the help of circuit diagrams.
- III.
- 1 Draw a cascode loaded MOS differential amplifier and explain its operation.
- Or
- 2 What are the important CMOS opamp parameters ? Define five of them and give their ideal and practical values.
- IV.
- 1 Draw an instrumentation amplifier using four opamps and explain the need for each opamp. Derive the expression for its voltage gain.
- Or
- 2 Draw a Wien Bridge oscillator using opamp and derive the expression for its frequency of oscillation. How is amplitude limiting done ?
- Or
- V.
- 1 Draw a second order active HPF and derive the expression for its cut off frequency. Explain its operation.
- Or
- 2 Draw BPF using Sallen-Key configuration and derive the expression for its band of elimination. Explain the operation.

(4 × 15 = 60 marks)