

D 1942

Name.....

Reg. No.....

**FIFTH SEMESTER B.Tech. (ENGINEERING) DEGREE EXAMINATION
DECEMBER 2004**

(New Scheme)

EC 2K 506 B/AI 2K 506 B—POWER ELECTRONICS

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

- I. (a) Explain in detail the power rating of SCR.
(b) Derive the expression for periodic time T of the UJT relaxation oscillator.
(c) Derive an expression for the average d.c. load voltage for single-phase fully controlled converter with (i) resistance load and (ii) inductance load.
(d) List the various PWM techniques. How do these differ from each other ?
(e) List the advantages and disadvantages of half-wave and single-phase a.c. regulator.
(f) Explain with suitable diagram, the operation of step-up d.c. chopper.
(g) Give the advantages and disadvantages of boost regulator.
(h) Write short notes on phase synchronization in UPS system.
- II. (a) Explain the various types of triggering (turning on) methods of SCR in detail. Which is the universal method and why ? (8 × 5 = 40 marks)
- (15 marks)
- Or*
- (b) With the help of neat structural diagram and suitable waveforms, explain the operation of insulated-gate BJT (IGBT). (15 marks)
- III. (a) Explain with the help of neat power-diagram and associated waveforms, the operation of a single-phase half-controlled converter with (i) Resistive load and (ii) Inductive load. (15 marks)
- (15 marks)
- Or*
- (b) Draw and explain the simple SCR series inverter circuit employing class A type commutation. Draw and discuss the important waveforms. State the limitations of this series inverter. (15 marks)
- IV. (a) Discuss the working of a two-stage sequence control of voltage regulators for both R and RL loads. What is the advantage of this regulator over a single-phase full-wave voltage regulator ? (15 marks)
- (15 marks)
- Or*
- (b) Draw and explain with suitable diagrams, the operation of a speed control of a d.c. shunt motor. (15 marks)
- V. (a) Explain with suitable circuit diagram and waveforms, the operation of Buck regulator. (15 marks)
- (15 marks)
- Or*
- (b) Explain with suitable block diagram, the operation of ON-line UPS system. (15 marks)
- marks)